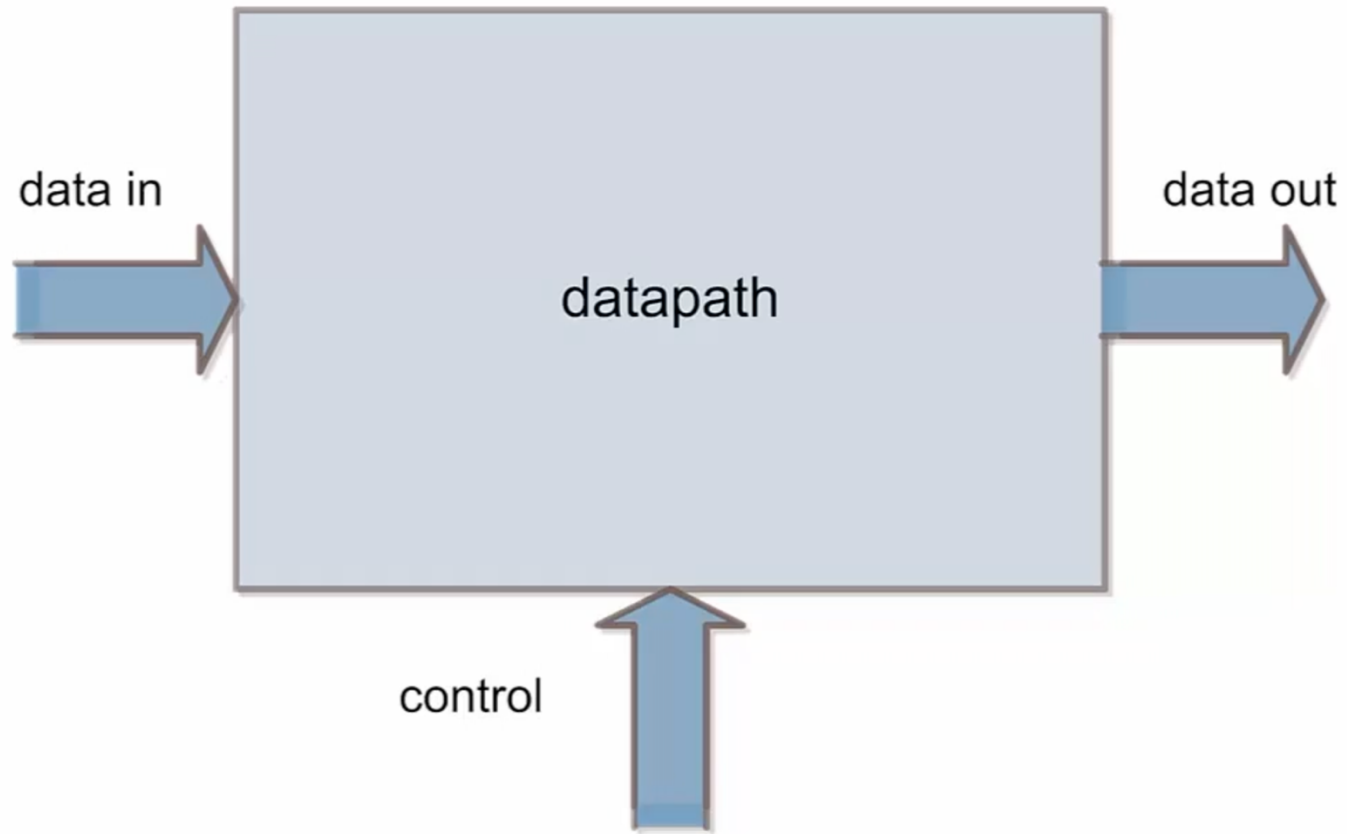






Digital Circuit Design

Li Bai


Data Path




Recall the multiplication

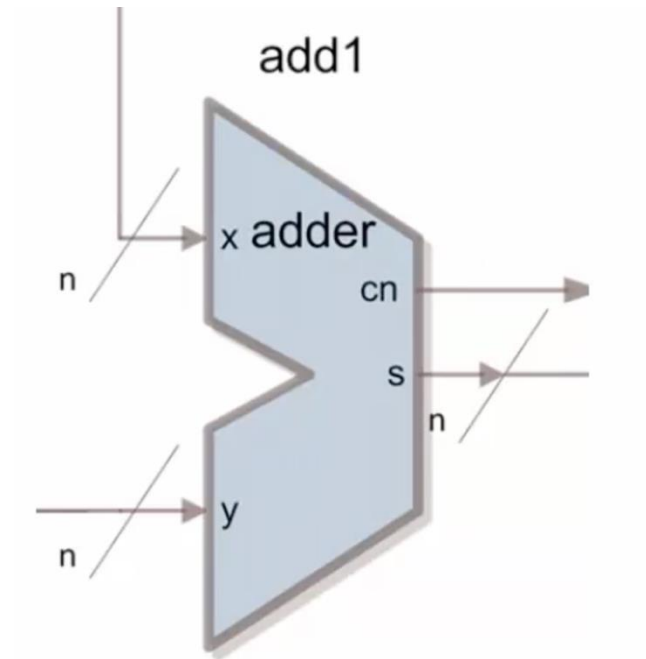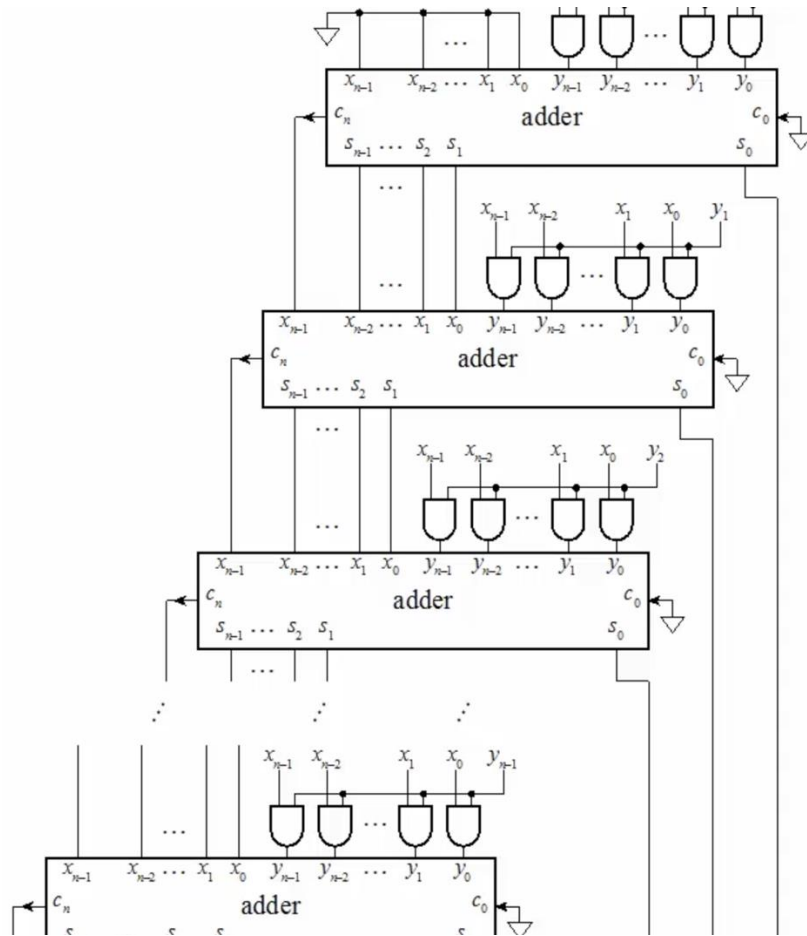


Shift only one bit and with x bus

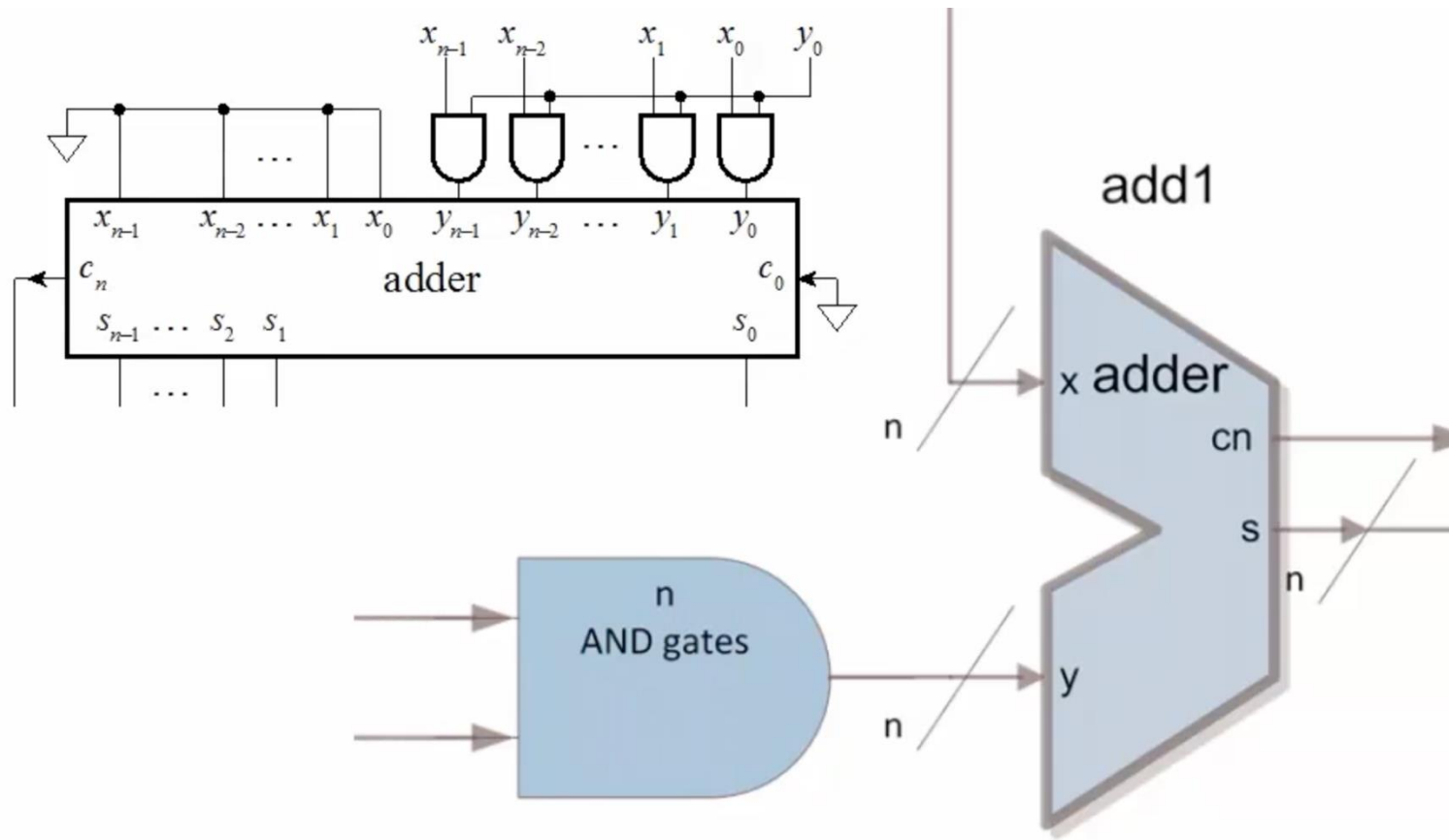


Use a n -bit shift register

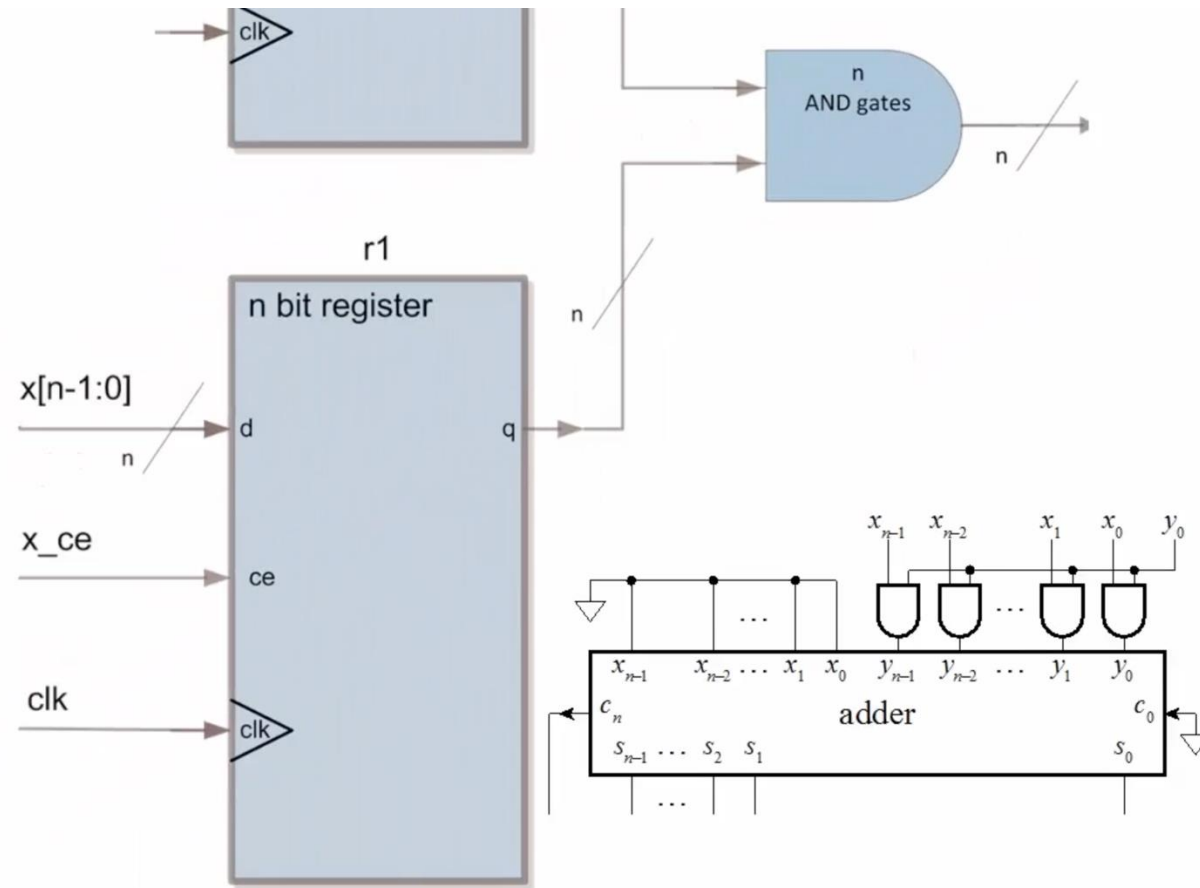

Shift y bus one bit at a time

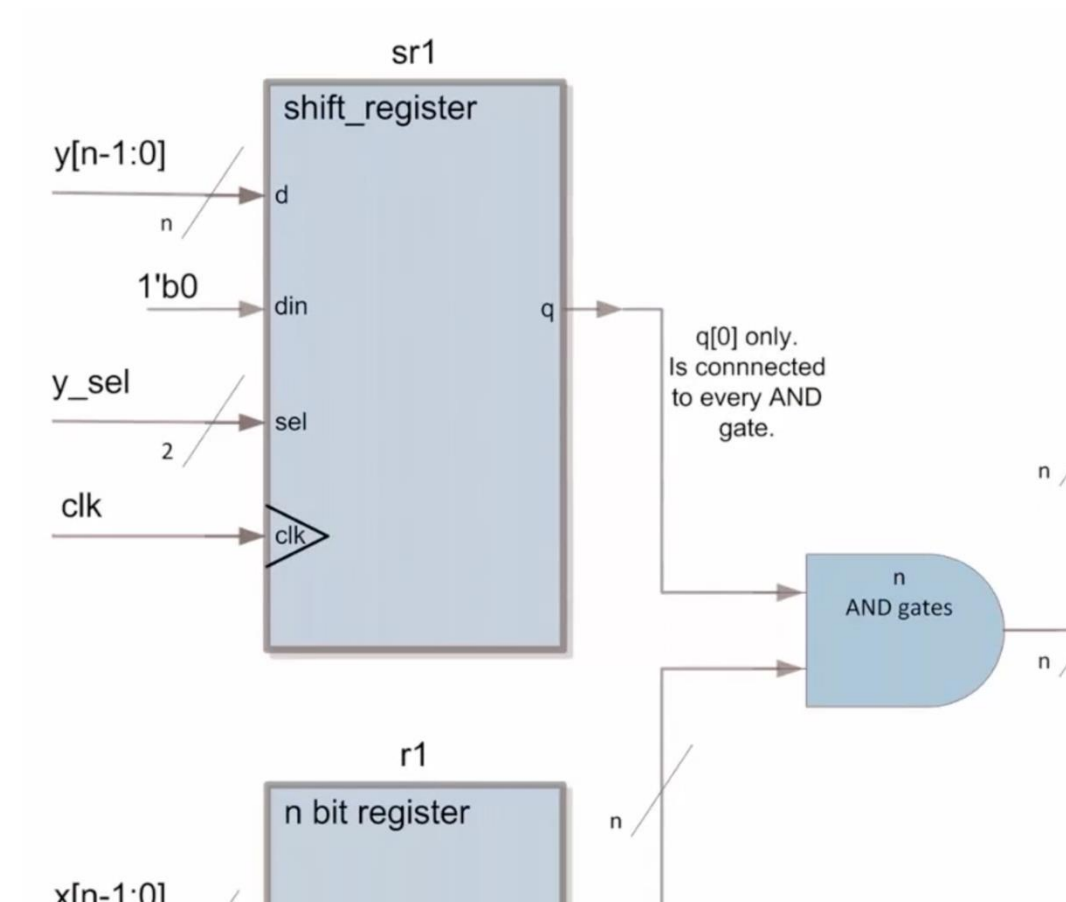

Why y_sel has 2-bit

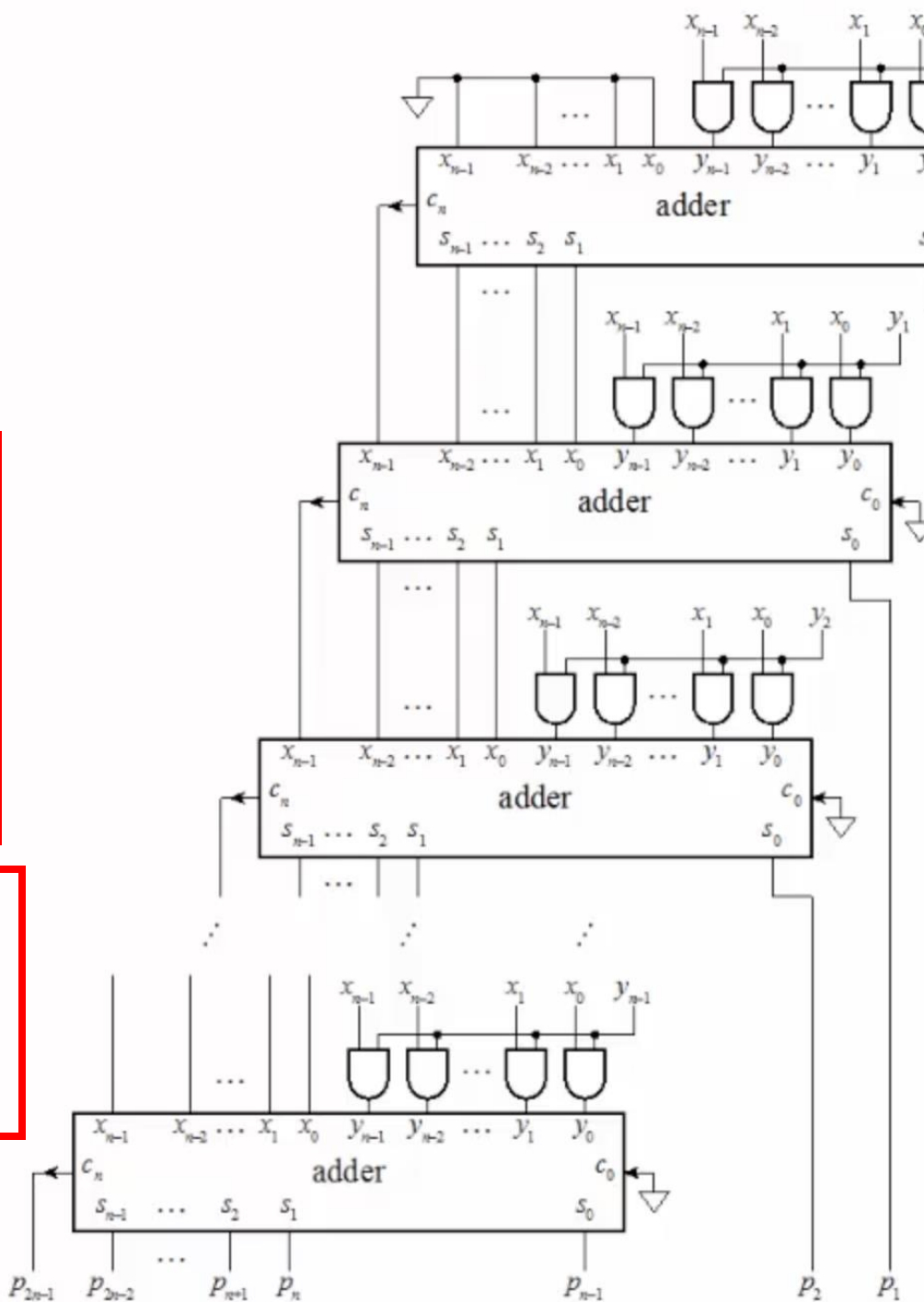




Advantage of a data path

- Use time to control data load and shift operation to achieve calculation
- You can use less number hardware
- Clock speed is important and instruction is important

Data Path for complex multiplication

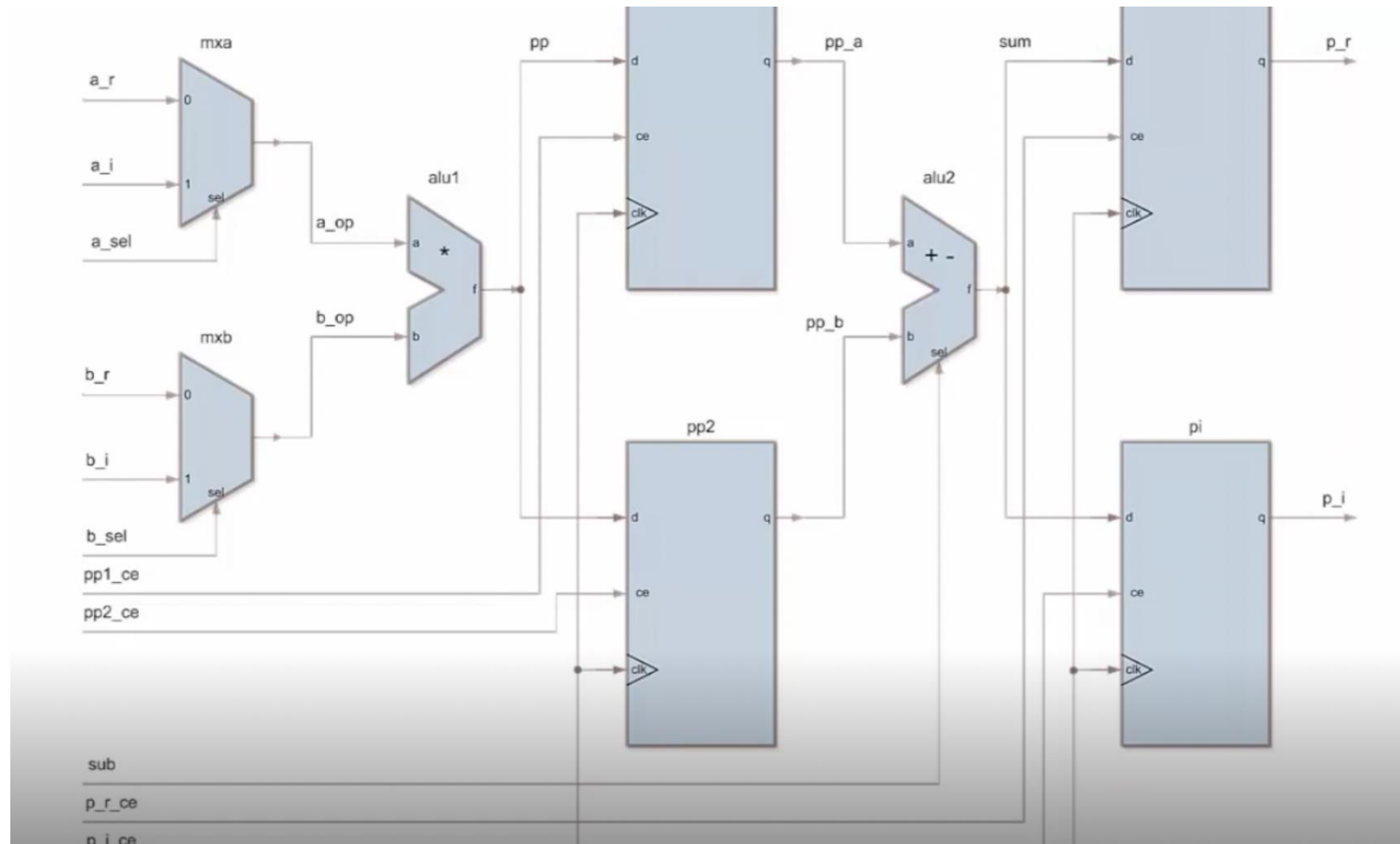


Data Path

Step	Operation
1	$a_r * b_r$ and store in register pp1
2	$a_i * b_i$ and store in register pp2
3	$(pp1) - (pp2)$ store in register pr
4	$a_r * b_i$ and store in register pp1
5	$a_i * b_r$ and store in register pp2
6	$(pp1) + (pp2)$ store in register pi

Step	a_sel	b_sel	pp1_ce	pp2_ce	sub	p_r_ce	p_i_ce
1	0	0	1	-	-	-	-
2	1	1	0	1	-	-	-
3	-	-	-	-	1	1	-
4	0	1	1	-	-	0	-
5	1	0	0	1	-	0	-
6	-	-	-	-	0	0	1

Step	a_sel	b_sel	pp1_ce	pp2_ce	sub	p_r_ce	p_i_ce
1	0	0	1	-	-	-	-
2	1	1	0	1	-	-	-
3	0	1	1	-	1	1	-
4	1	0	0	1	-	0	-
5	-	-	-	-	0	0	1

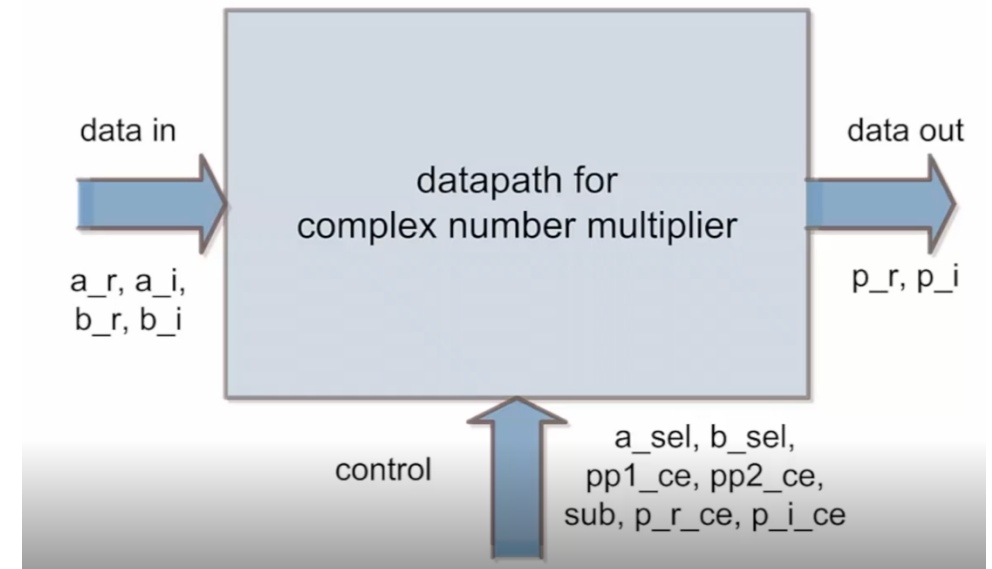


→ Instruction sets

Instruction set and processors

- CISC (Complex Instruction Set Computer)
 - Intel processor
 - Power PC processor
 - Western Digital
- RISC (Reduced Complex Instruction Set Computer)
 - ARM processor
 - Raspberry pi
 - Smart Phone
 - AVR processor (Alf and Vegard's RISC
 - (Ateml- ECE3612)
- Apple
 - Power pc -> Intel processor -> A14 Bionic -> M1 Processor

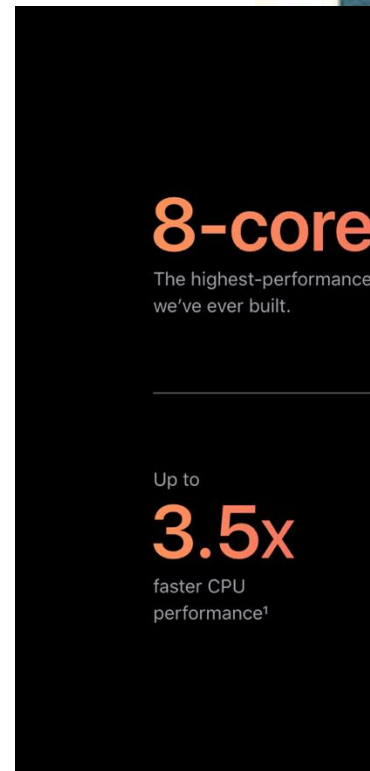Q&A With Co-Creator of the 6502 Processor – IEEE Spectrum



Robert Noyce




Born Robert Norton Noyce
December 12, 1927
[Burlington, Iowa](#)

Died June 3, 1990 (aged 62)
[Austin, Texas](#)


Alma mater [Grinnell College](#)
[Massachusetts Institute of Technology](#)

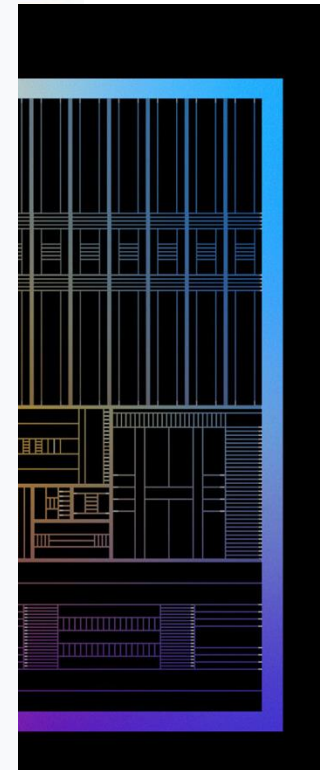Occupation Co-founder of [Fairchild Semiconductor](#) and [Intel](#)




Scholarships | Temple University College of Engineering

FSM - basic example

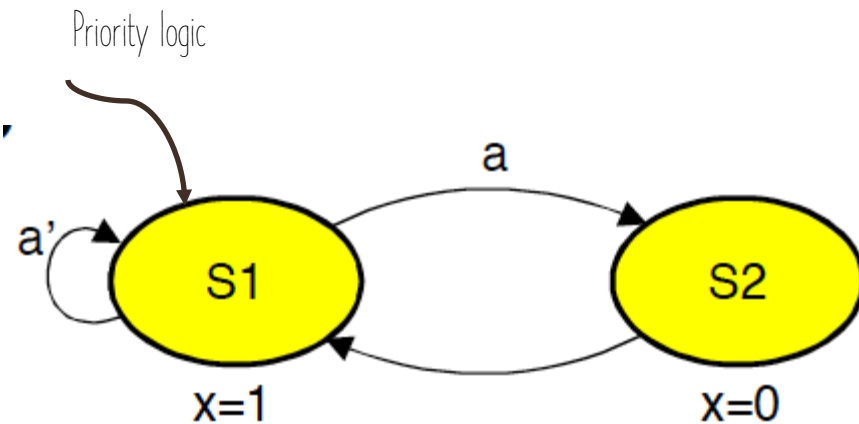


```
module simple_fsm (input a, output reg x);
    reg state, next_state;
    parameter S1=0, S2=1;
    // synchronous block
    always @(posedge clk) begin
        state <= next_state;
    end
    // combinational block
    always @* begin
        // defaults
        next_state = state;
        x = 0;
        // regular logic
        case(state)
            S1: begin
                x = 1;
                if(a==1) begin
                    next_state = S2;
                end // end of if
            end // end of S1
            S2: next_state = S1;
        endcase
        // priority logic
    end // end of always
endmodule
```

Example

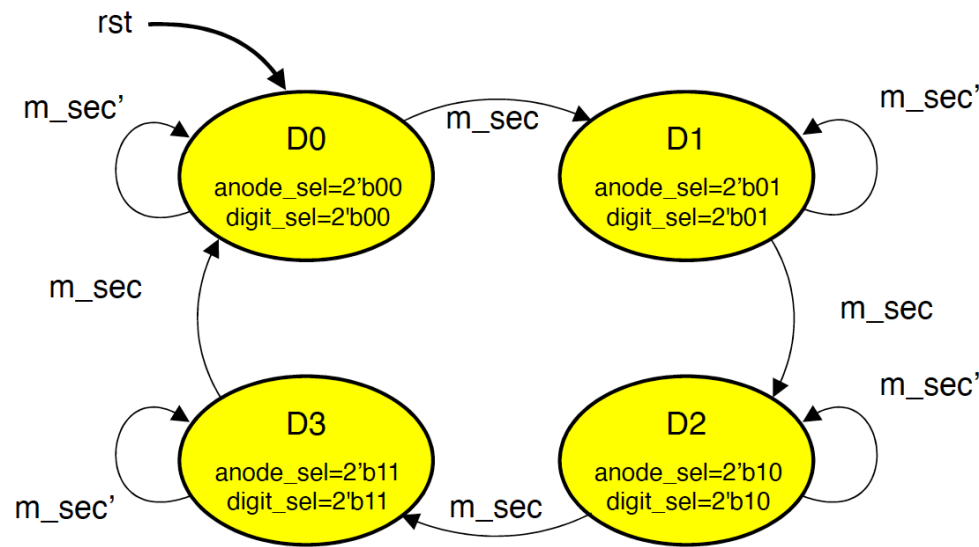

```
module display_fsm (input m_sec, input
rst, output reg [1:0] anode_sel, output
reg [1:0] digit_sel);
    reg state, next_state;
    parameter S1=0, S2=1;
    // synchronous block
    always @(posedge clk) begin
        state <= next_state;
    end
    // combinational block
    always @* begin
        // defaults
        next_state = state;
        x = 0;
        // regular logic
        case(state)
            S1: begin
```

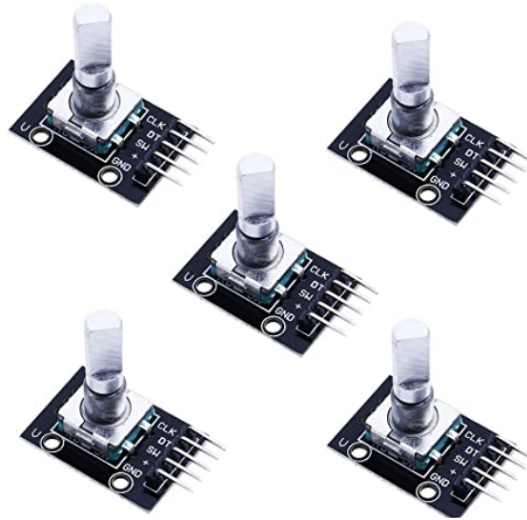

SongHe 5pcs KY-040 Rotary Encoder Brick Sensor Module Development for Arduino AVR PIC

Brand: Teyleten Robot

★★★★★ 5 ratings

Price: \$5.82 ✓prime & FREE Returns

S Searching ..



Specifications for this item



Brand Name
Teyleten Robot



Quadrature Rotary Encoder

<https://www.amazon.com/SongHe-KY-040-Encoder-Development-Arduino/dp/B087ZQLLWQ>

Rotary Encoder

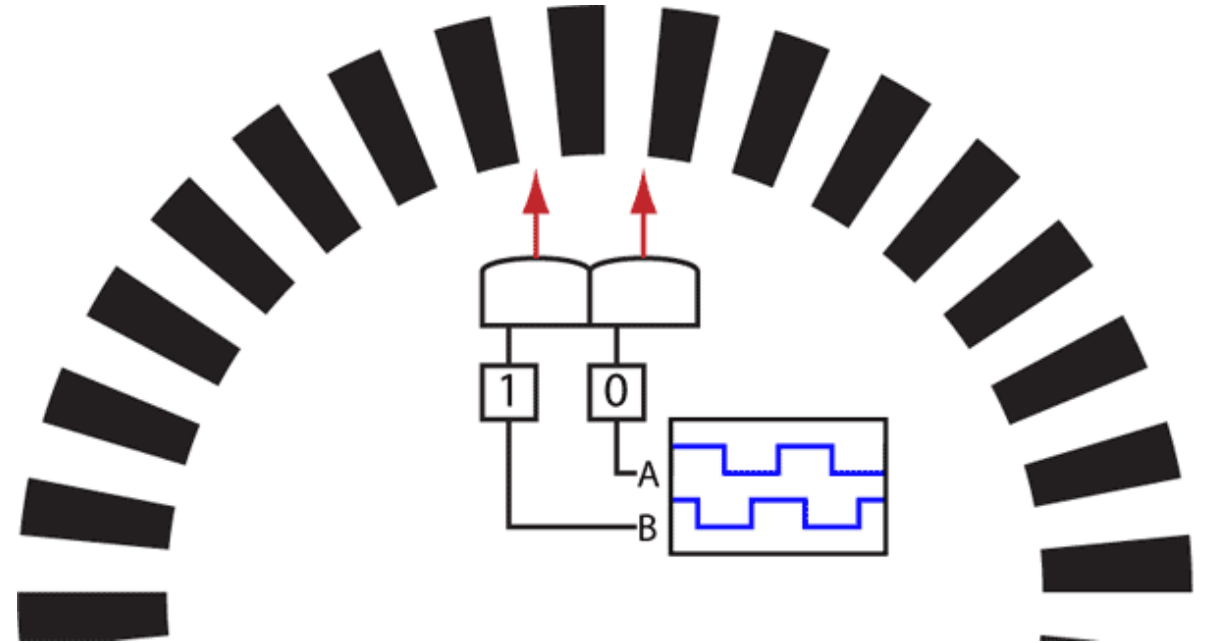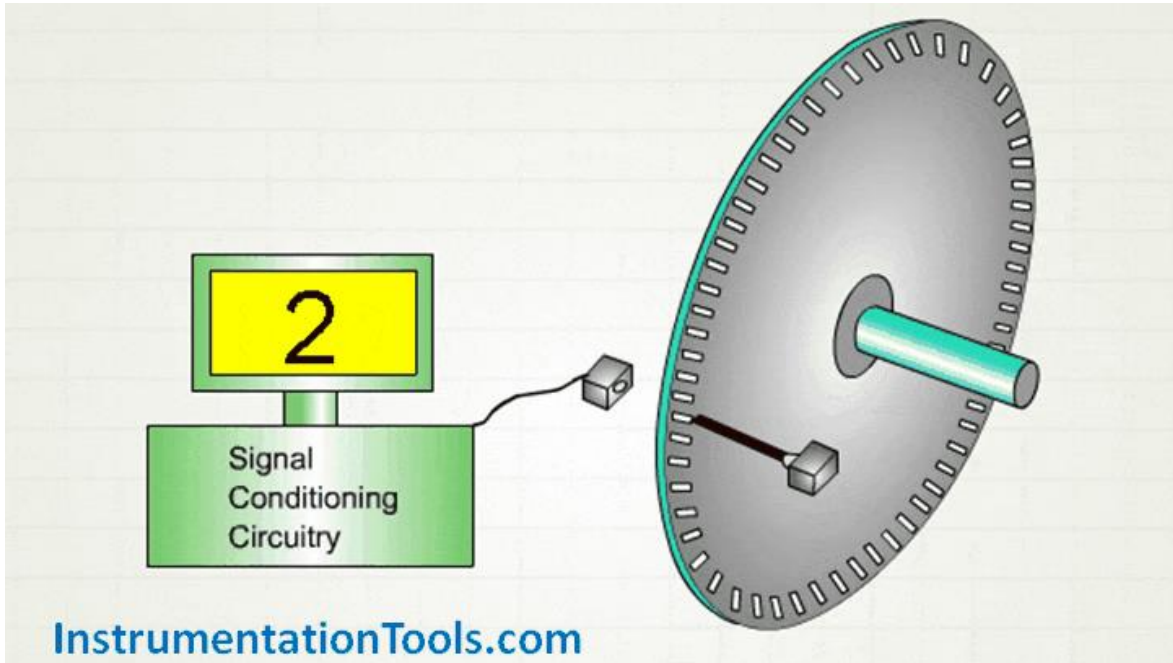

Rotatory Encoder Type

Electronics

Category

Forum

Blog

Support

Ordering

Distributors

About

Contact

Pololu Metal Gearmotors » 25D mm Metal Gearmotors » 6V Low-Power (LP) 25D mm Gearmotors » 34:1 Metal Gearmotor 25Dx52L mm LP 6V with 48 CPR Encoder



Pololu item #: 2284

39 in stock

Brand: Pololu

Status: Active and Preferred

Free shipping in USA

Price break

Unit price (US\$)

1

34.95

10

31.46

Quantity: 1

Add to cart

backorders allowed

Add to wish list

www.pololu.com



This gearmotor consists of a **low-power, 6 V** brushed DC motor combined with a **34.014:1** metal spur gearbox, and it has an integrated 48 CPR quadrature encoder on the motor shaft of the gearbox's output shaft. The gearmotor is cylindrical, with a output shaft is 4 mm in diameter and extends 12.5 mm from the face

Key specs at 6 V: 170 RPM and 250 mA free-run, 50 oz-in (3.5 kg

You can use the following selection boxes to choose from all of our

☐ Compare Product


[Add To Project](#) | [Add Notes](#)

Specifications


Product Attribute	Attribute Value	Search Similar
Manufacturer:	Bourns	<input type="checkbox"/>
Product Category:	Encoders	<input checked="" type="checkbox"/>
RoHS:	 Details	
Series:	PEC11R	<input type="checkbox"/>
Mounting Style:	Panel Mount	<input type="checkbox"/>
Product:	Mechanical Encoders	<input type="checkbox"/>
Type:	Incremental	<input type="checkbox"/>
Resolution:	24 PPR	<input type="checkbox"/>
Technology:	Rotary	<input type="checkbox"/>
Number of Detents:	24 Detent	<input type="checkbox"/>

Types of quadrature encoding


X1:

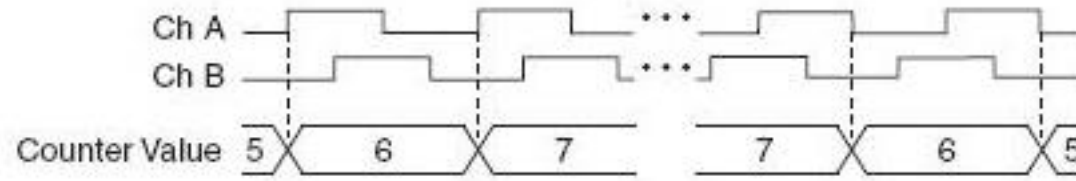




X2:

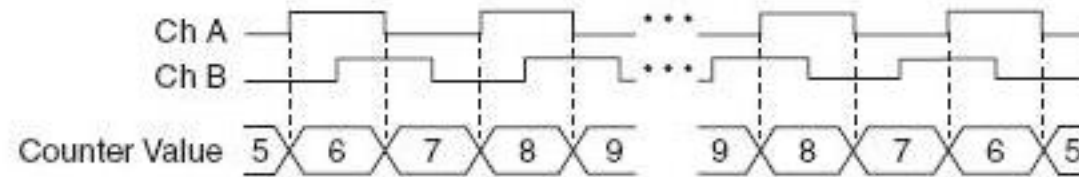

X4:


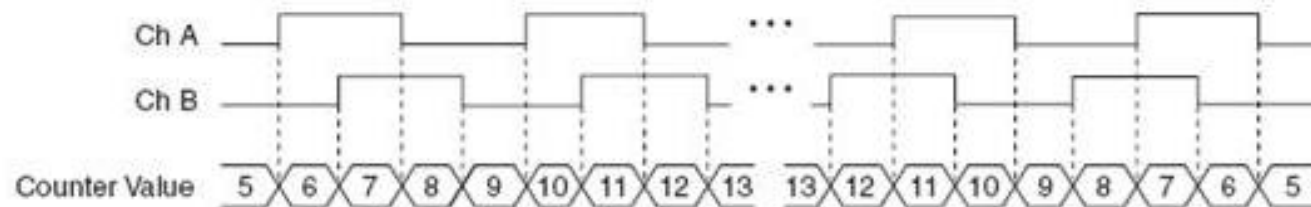


Connection of QD Rotary Encoder

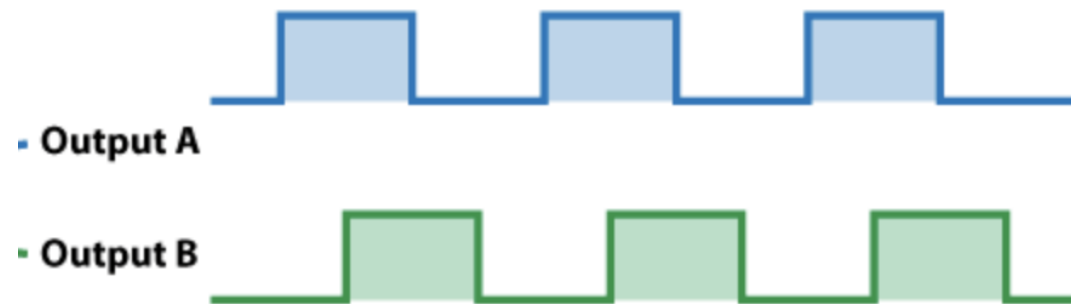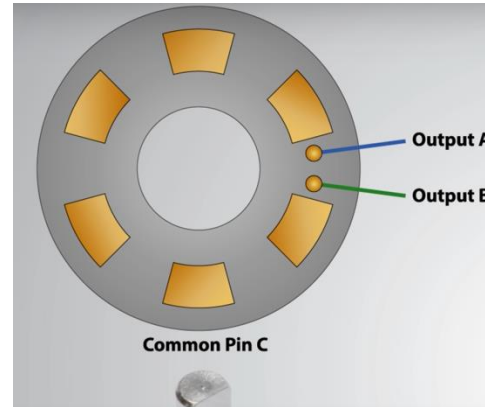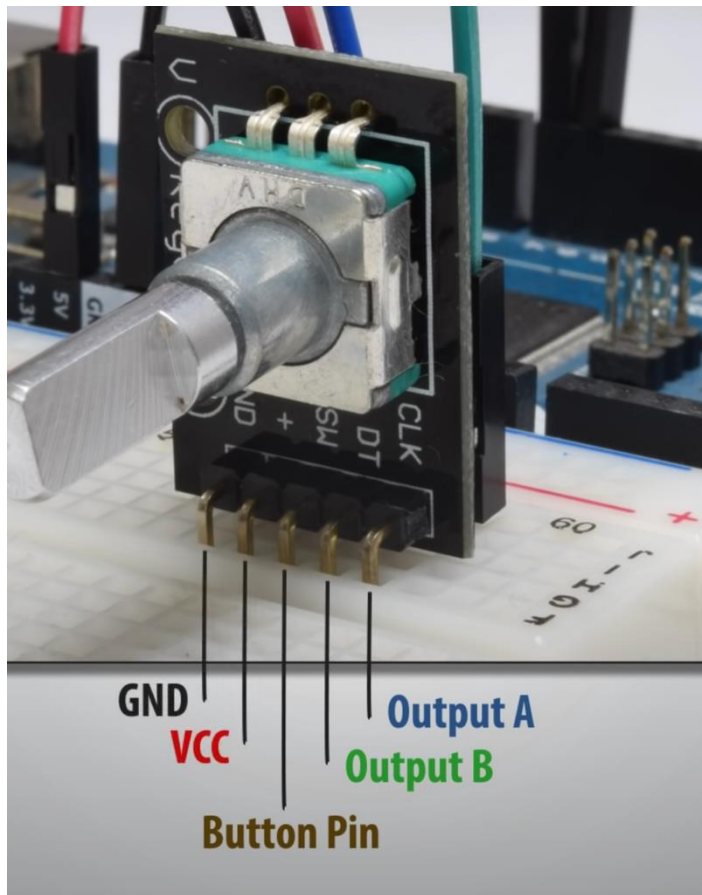

<https://howtomechatronics.com/tutorials/arduino/rotary-encoder-works-use-arduino/>

How to count (x4)...

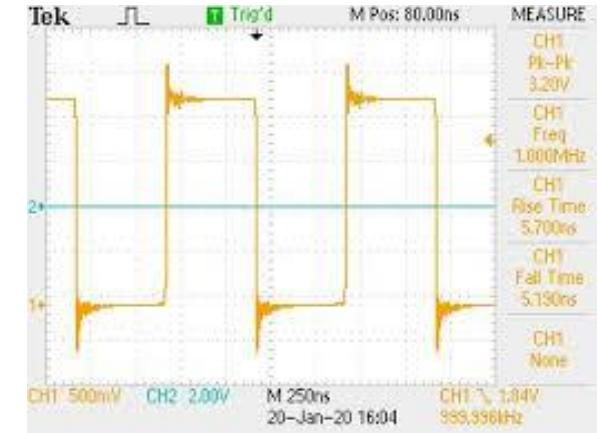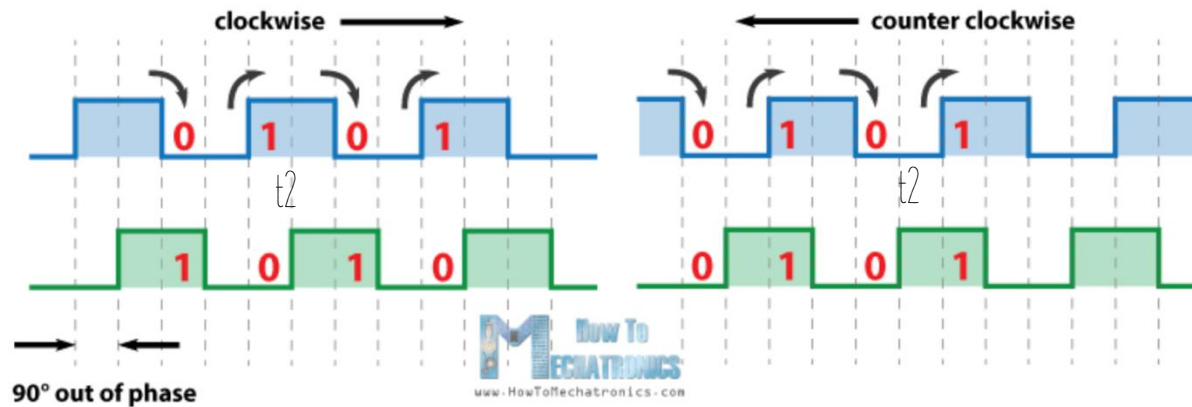

State [AB]	Next State [AB]	action
10	11	increment
11	01	increasement
01	00	increasement
00	10	increasement


State [AB]	Next State [AB]	action
		decrement
		decrement
		decrement
		decrement

State [AB]	Next State [AB]	action
		hold
		hold
		error
		error


List all conditions

q_prev_a	q_prev_b	q_now_a	q_now_b	quad_ctl	function
0	0	0	0	2'b00	Hold
0	1	0	1		
1	0	1	0		
1	1	1	1		
0	0	0	1	2'b01	Count up
0	1	1	1		
1	1	1	0		
1	0	0	0		
0	0	1	0	2'b10	Count down
1	0	1	1		
1	1	0	1		
0	1	0	0		
0	0	1	1	2'b11	Error
0	1	1	0		
1	0	0	1		
1	1	0	0		


rst	carry_in	up_down	bcd	next_bcd	carry_out	Function
1	x	x	x	4'd0	x	Reset
0	0	x	4'd0 to 9	hold bcd	0	Hold
0	1	1	4'd0 to 8	bcd + 1	0	Count up
0	1	1	4'd9	4'd0	1	
0	1	0	4'd1 to 9	bcd - 1	0	Count down
0	1	0	4'd0	4'd9	1	

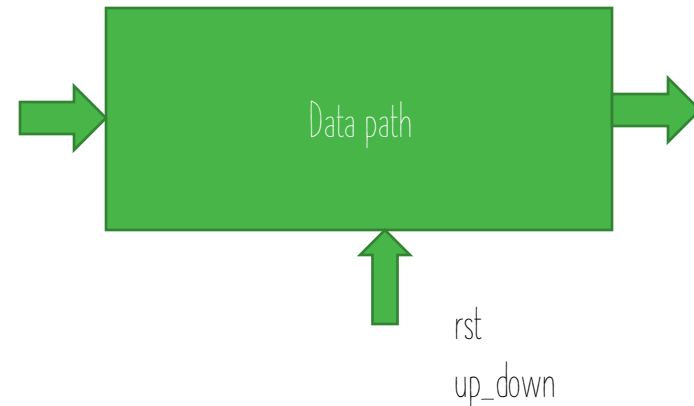


Section 2: Design for up_down_count_dp

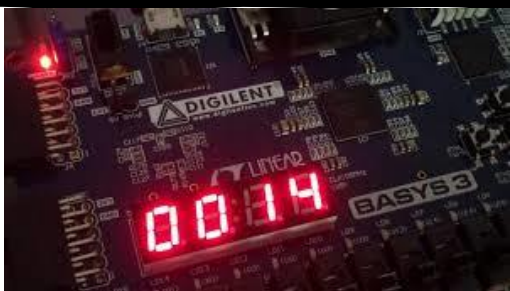


rst	carry_in	up_down	bcd	next_bcd	carry_out	Function
1	x	x	x	4'd0	x	Reset
0	0	x	4'd0 to 9	hold bcd	0	Hold
0	1	1	4'd0 to 8	bcd + 1	0	Count up
0	1	1	4'd9	4'd10	1	
0	1	0	4'd1 to 9	bcd - 1	0	Count down
0	1	0	4'd0	4'd9	1	

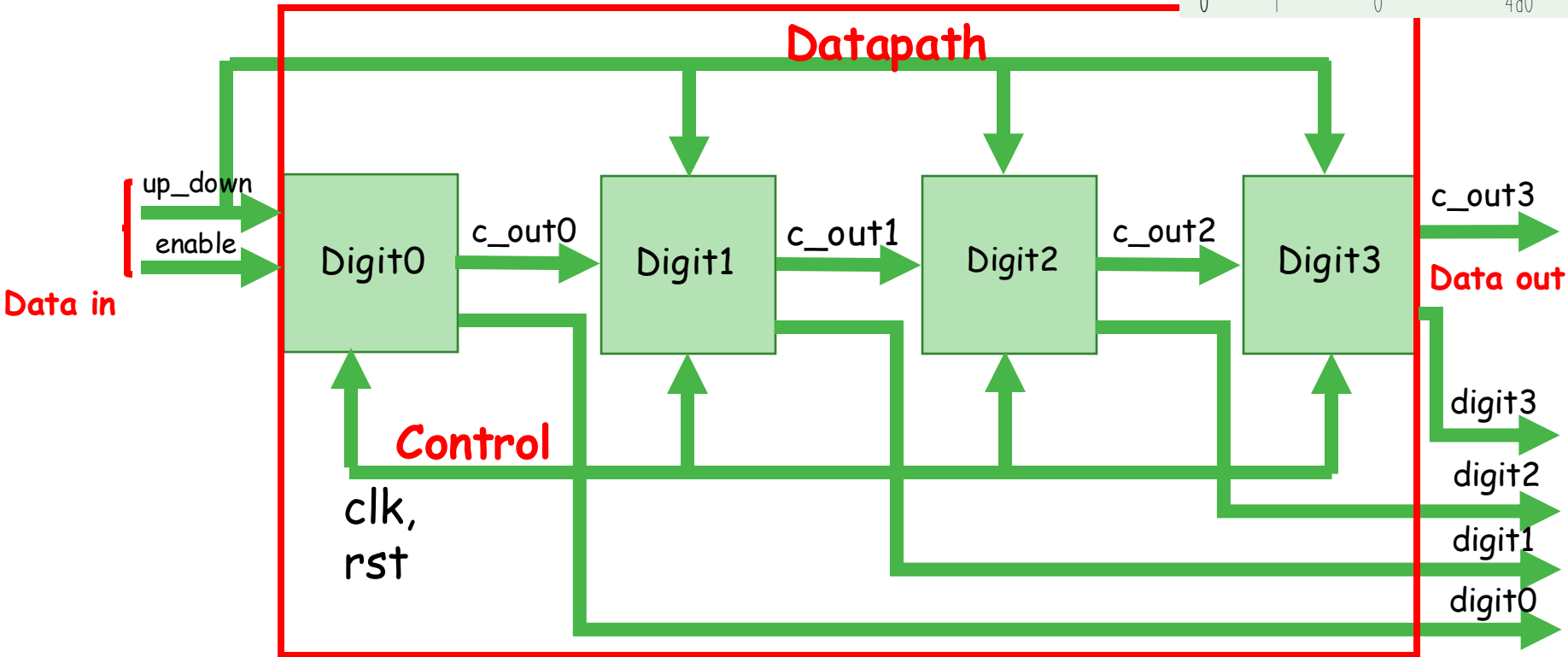


Recall the lab 7

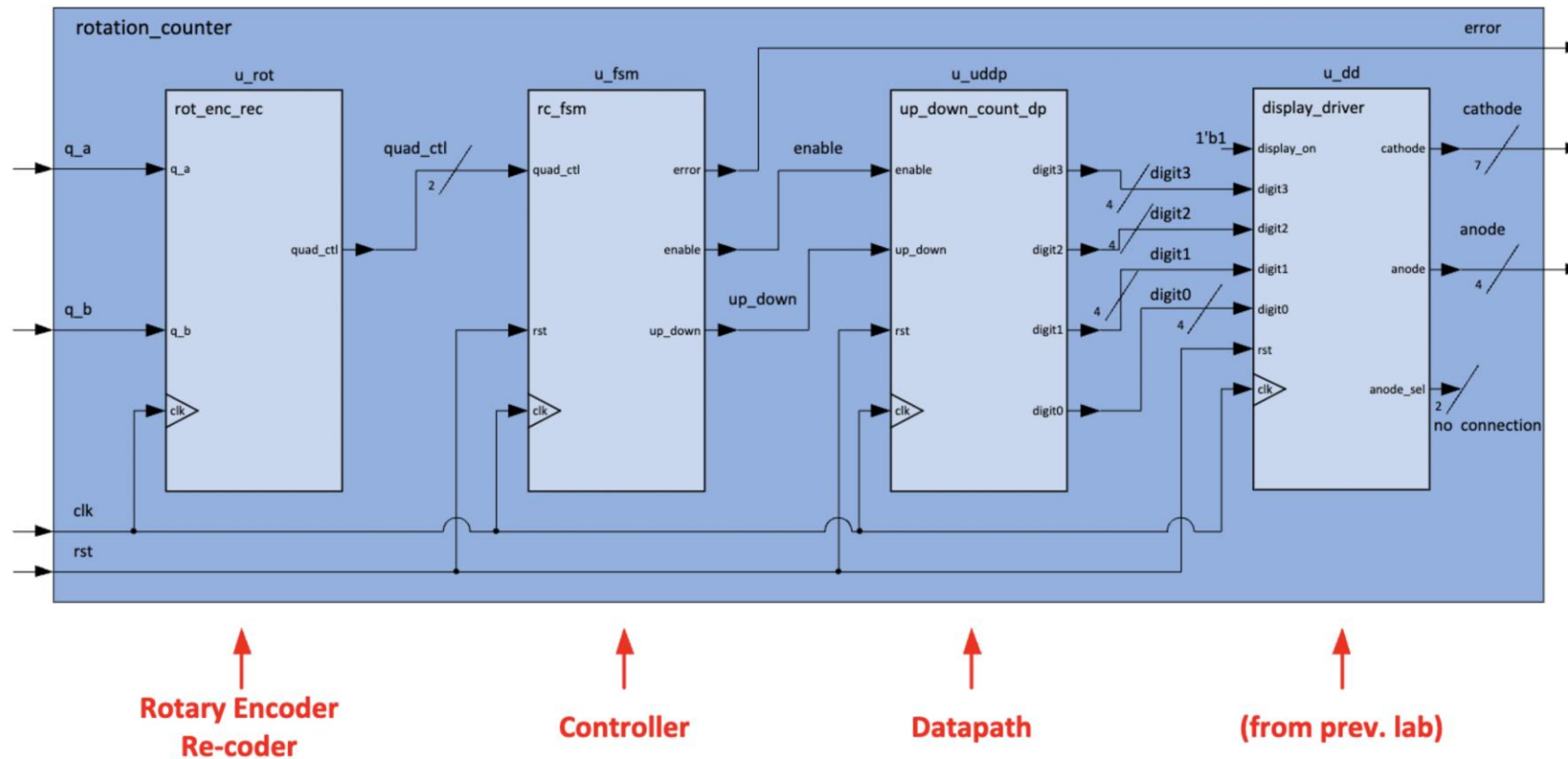

Create a datapath

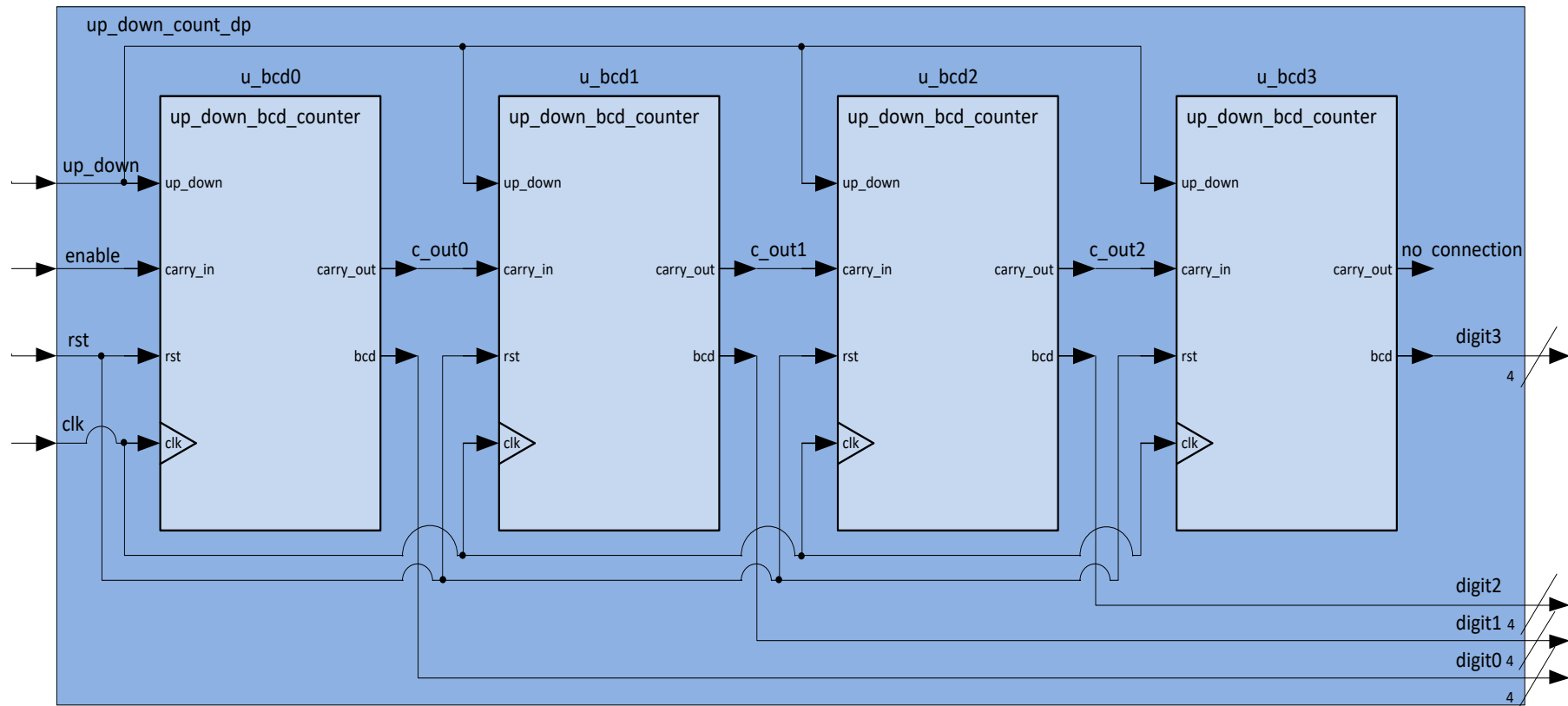


Design for up_down_bcd_counter

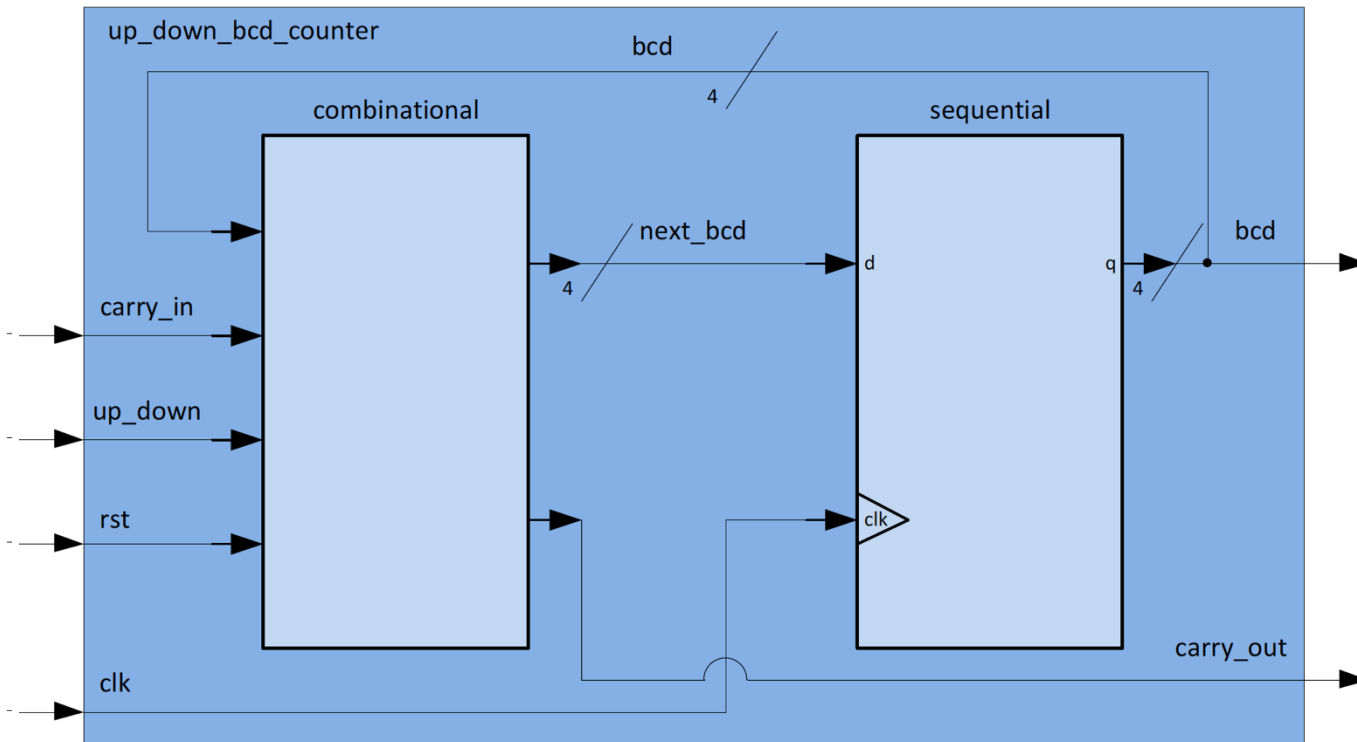

Bcd_counter combinational logic

<i>carry_in</i>	<i>up_down</i>	<i>bcd</i>	<i>next_bcd</i>	<i>carry_out</i>	Function
x	x	x	4'd0	x	Reset
0	x	4'd0 to 9	hold bcd	0	Hold
1	1	4'd0 to 8	bcd + 1	0	Count up
1	1	4'd9	4'd10	1	
1	0	4'd1 to 9	bcd - 1	0	Count down
1	0	4'd0	4'd9	1	

Counter Block Diagram

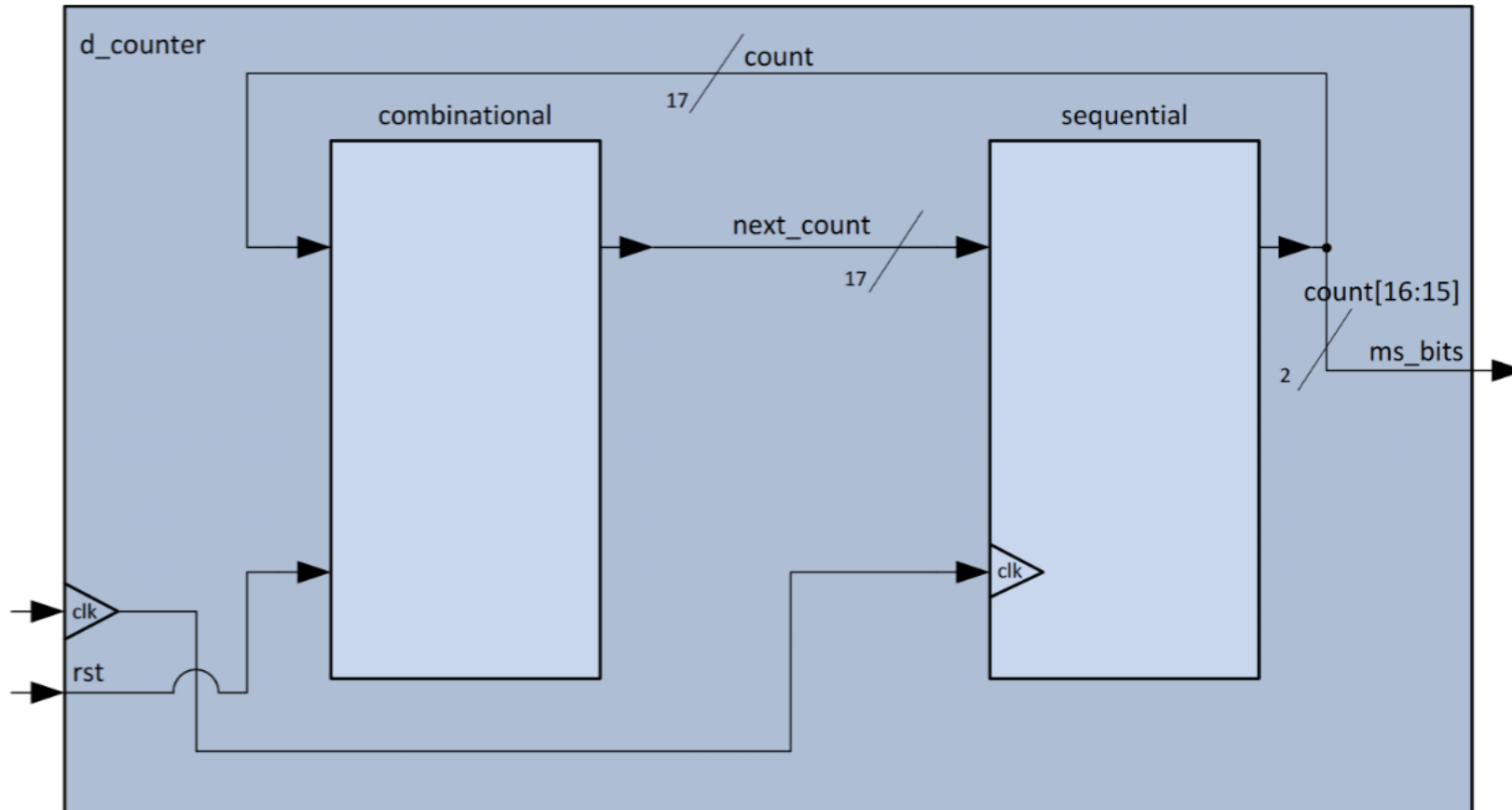

```
// Code your design here
`timescale 1ns/1ns
module cd_counter(output reg ms_bits, input wire clk, input wire rst);


    reg [16:0] count, next_count;

    // synchronous logic
    always @(posedge clk) begin
        count <= next_count;
    end

    // combinational logic
    always @* begin
        // defaults
        // count down
        next_count = count - 1;
        // priority logic
        if (rst == 1) next_count = 0;
    end


    assign ms_bits=count[16:15];
endmodule
```

Stopwatch_dp

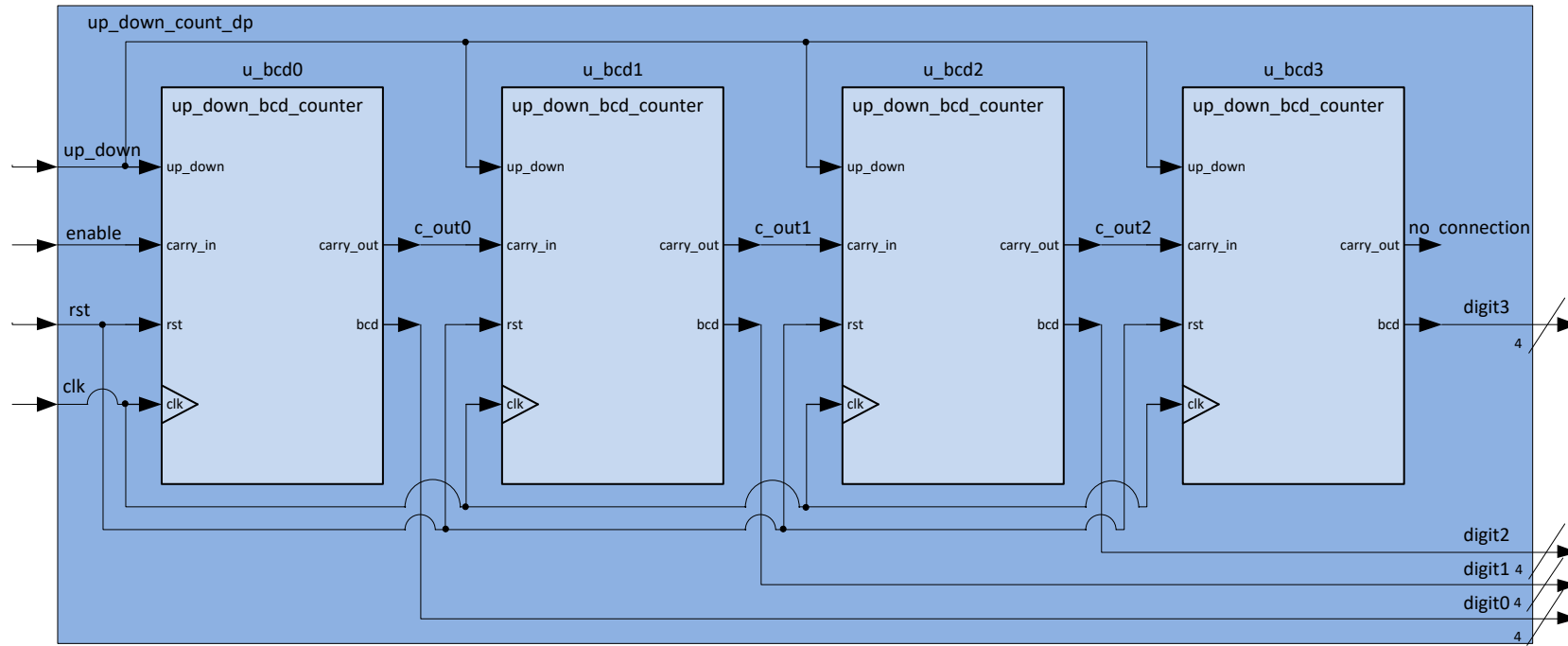



Create stop watch

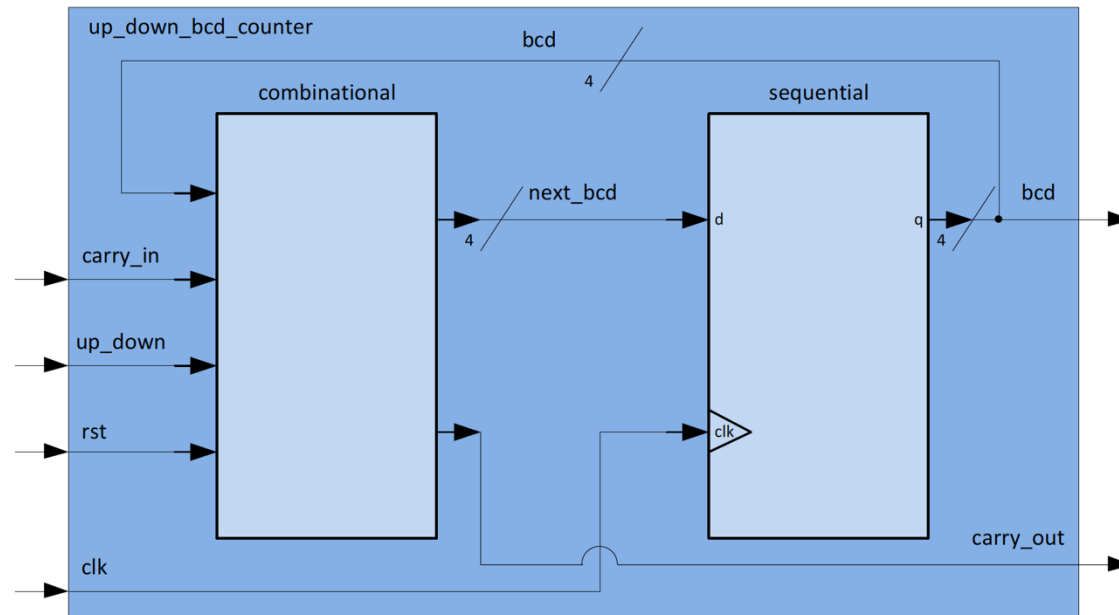

Think about 1 second watch with 50 MHz clock

Think about 1 second watch with 50 MHz clock

Onenote
