

The background features a dark, textured surface with numerous out-of-focus, warm-toned bokeh lights scattered across the upper half. A large, vibrant green, rounded shape on the right side serves as a container for the title and author information.

Digital Circuit Design

Li Bai

Module 6

- Non integer representation
 - Fix-point
 - Float-point
- Multiplication process
 - Bit-wise multiplication
 - Shift operation (represent numbers as sum of multiple of 2^n)
 - Use multiplication IP core (block diagram instantiation)
- Sequential Logic
 - S/R Latch
 - D latch
 - D flip-flop

Fix-point representation

- m:f representation
- Example: for an n -bit number with m -bits "before" the decimal point (the integer component) and f -bits for the fraction
($n = m + f$):

Float point representation

- Mantissa and exponents
- Signed bit
- Mantissa (map to number decimal number 1-9)
- Exponents using excess form
 - 8-bit represent 256
 - excess form $(-127, 127)$ mapped to 8'b0 to 8'b1

IEEE 754-1985 Standard

32-bit floating point number

31	30	29	...	24	23	22	21	...	1	0
sign	exponent					mantissa				

64-bit floating point number

63	62	61	...	53	52	51	50	...	1	0
sign	exponent					mantissa				

Example

Normalized Form

Let's illustrate with an example, suppose that the 32-bit pattern is 1 1000 0001 011 0000 0000 0000 0000 0000, with:

- $S = 1$
- $E = 1000\ 0001$
- $F = 011\ 0000\ 0000\ 0000\ 0000\ 0000$

In the *normalized form*, the actual fraction is normalized with an implicit leading 1 in the form of $1.F$. In this example, the actual fraction is $1.011\ 0000\ 1.375D$.

The sign bit represents the sign of the number, with $S=0$ for positive and $S=1$ for negative number. In this example with $S=1$, this is a negative number, i.e., -1


In normalized form, the actual exponent is $E-127$ (so-called excess-127 or bias-127). This is because we need to represent both positive and negative exponent scheme could provide actual exponent of -127 to 128. In this example, $E-127=129-127=2D$.

Hence, the number represented is $-1.375 \times 2^2 = -5.5D$.

Binary multiplication

- Convert one of the multiplication number into binary, then do the shift <<
- Example: $A * 10 = A * 8 + A * 2 = A \ll 3 + A \ll 1$

Multiplication IC

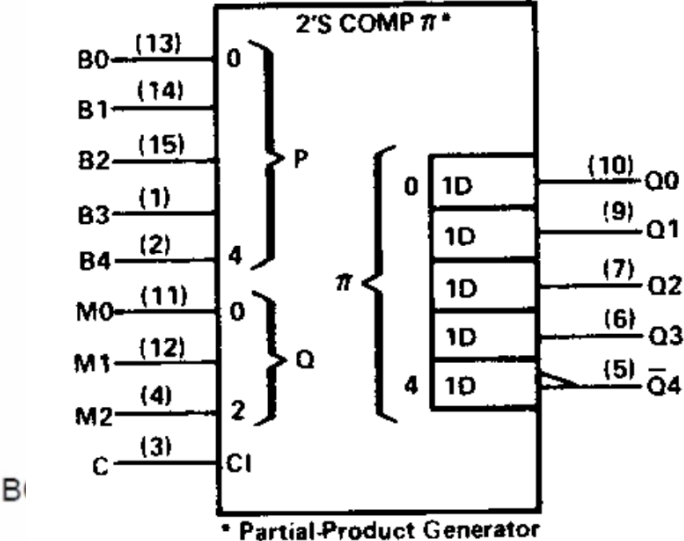

SN54LS261


[17:0]

18_021205

FUNCTION TABLE


INPUTS				OUTPUTS				
LATCH CONTROL C	MULTIPLIER			$\bar{Q}4$	Q3	Q2	Q1	Q0
	M2	M1	M0	$\bar{Q}4$	Q3	Q2	Q1	Q0
L	X	X	X	$\bar{Q}4_0$	Q3_0	Q2_0	Q1_0	Q0_0
H	L	L	L	H	L	L	L	L
H	L	L	H	$\bar{B}4$	B4	B3	B2	B1
H	L	H	L	$\bar{B}4$	B4	B3	B2	B1
H	L	H	H	$\bar{B}4$	B3	B2	B1	B0
H	H	L	L	B4	$\bar{B}3$	$\bar{B}2$	$\bar{B}1$	$\bar{B}0$
H	H	L	H	B4	$\bar{B}4$	$\bar{B}3$	$\bar{B}2$	$\bar{B}1$
H	H	H	L	B4	$\bar{B}4$	$\bar{B}3$	$\bar{B}2$	$\bar{B}1$
H	H	H	H	H	L	L	L	L

Multiplication IC

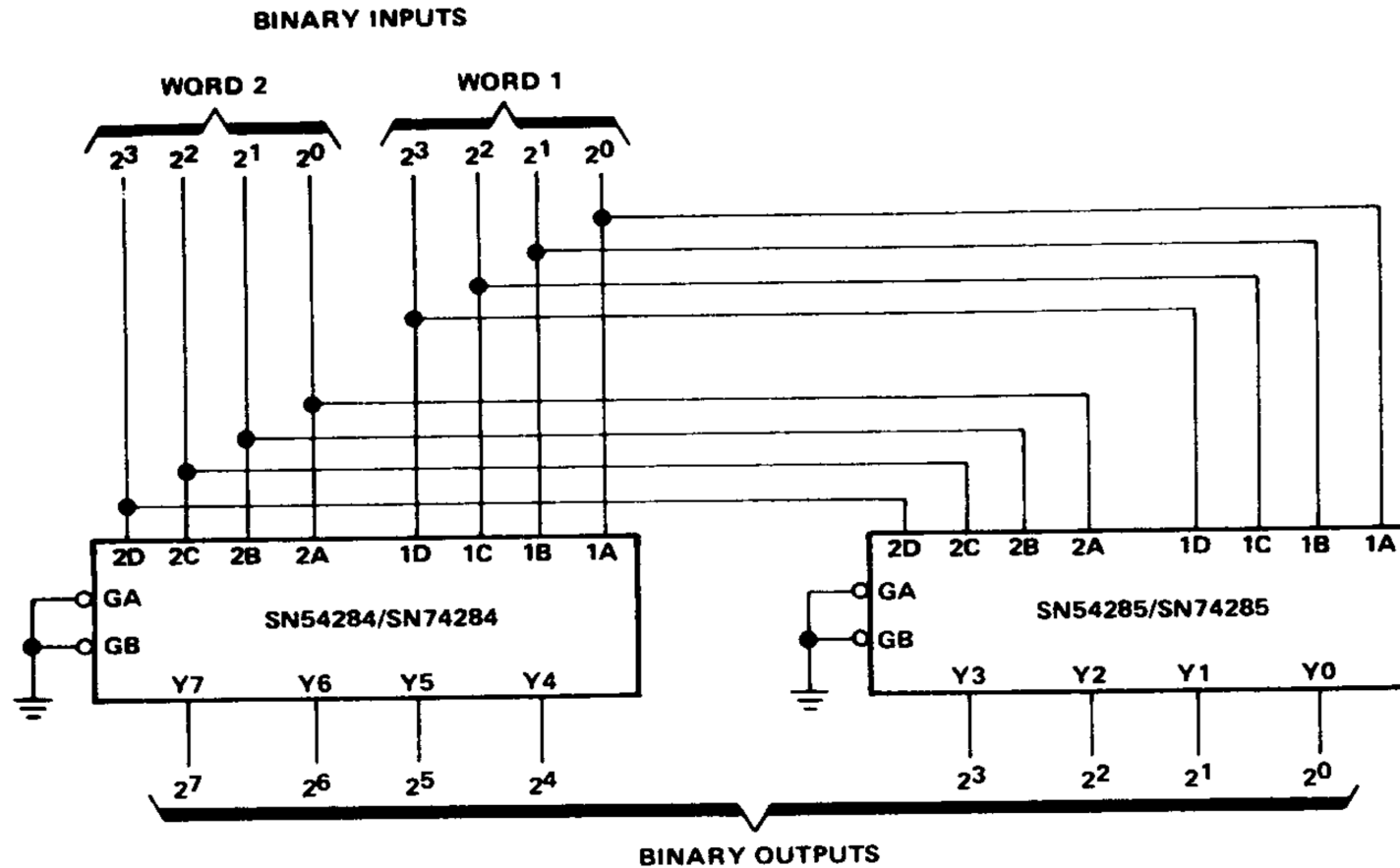


Another one ...


Pinout

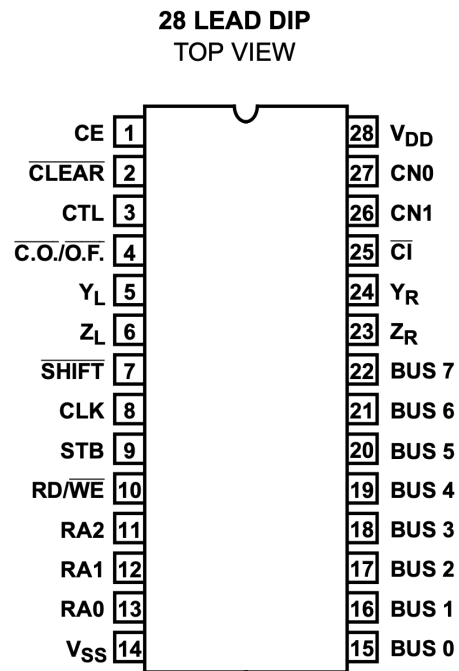

Circuit Configuration

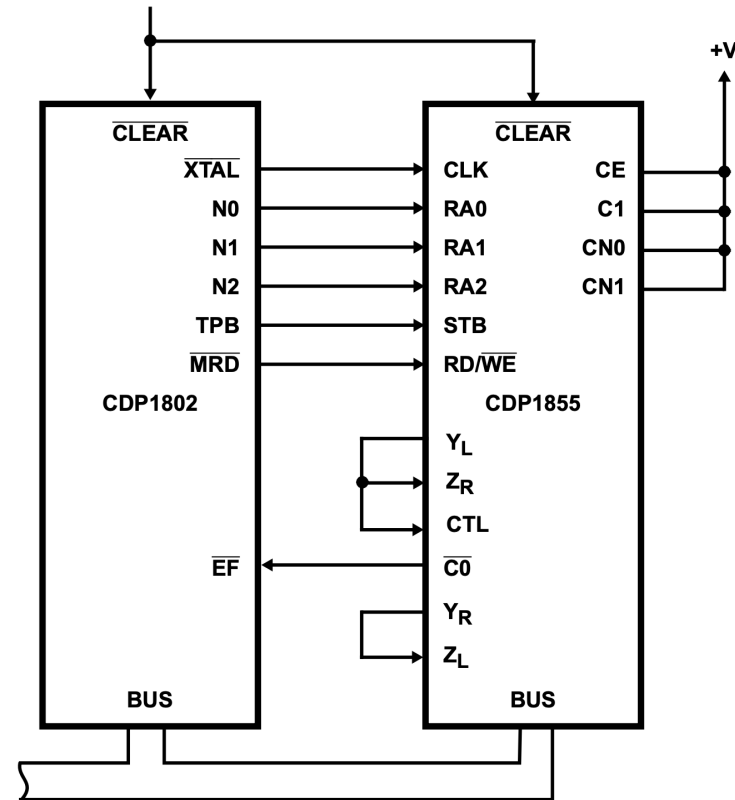


SR Latch

 


$$Q_a = \sim Q_b$$

S	R	Q_a	Q_b	Condition
0	0	0/1	1/0	Hold
0	1	1	0	Reset
1	0	0	1	Set
1	1	0	0	Illegal

Level Sensitive SR Latch

 


C	S	R	Q	Condition
0	x	x	1/0	Hold
1	0	0	1/0	Hold
1	0	1	0	Reset
1	1	0	1	Set
1	1	1	0	Illegal

 

C	D	Q	Condition
0	x	1/0	Hold
1	0	0	Q follows D
1	1	1	


Edge Sensitive D-Latch

D Flip-Flop


 


Clk	D	Q	Condition
\uparrow	X	Q_p	Hold
\uparrow	0	0	Q follows D
\uparrow	1	1	


Edge Trigger Symbol

 

  
Symbol for rising-edge triggered D flip-flop



 Symbol for falling-edge triggered D flip-flop




Edge Sensitive D-Latch


 


Clk	D	Q	Condition
\uparrow	X	Q_p	Hold
\uparrow	0	0	Q follows D
\uparrow	1	1	

Edge Trigger Symbol

 

  Symbol for rising-edge triggered D flip-flop



Symbol for falling-edge triggered D flip-flop

