

The background features a dark, textured surface with numerous out-of-focus, warm-toned circular lights (bokeh) scattered across the upper half. A large, solid green shape, resembling a stylized leaf or a speech bubble, is positioned in the lower right quadrant. The title text is centered within this green shape.

Digital Circuit Design

Li Bai

Module 8

- Counter/Divider
 - Master clock with a frequency and convert it to another frequency.
- Ripple counter
- Counter IC

Clock stimulus in verilog

- Generate a clock
- Timescale (resolution)
- 1MHz clock


```
`timescale 1ns/1ns
```

```
// generate the clock stimulus  
always begin  
    clk = 0;  
    #5;  
    clk = 1;  
    #5;  
end
```

timescale compiler directive

```
// or browse examples  
'timescale 1ns/1ns // define the time unit resolution and  
precision
```

Time resolution and precision

 


There are only **three valid magnitudes** for use in `time_unit` arguments. They are:

`1`, `10`, and `100`.


<https://www.edaplayground.com/x/CJEF>

Valid Time unit (in code)	Corresponding real-world time unit
s	seconds
ms	milliseconds
us	microseconds (µs)
ns	nanoseconds
ps	picoseconds
fs	femtoseconds

General sequential logic

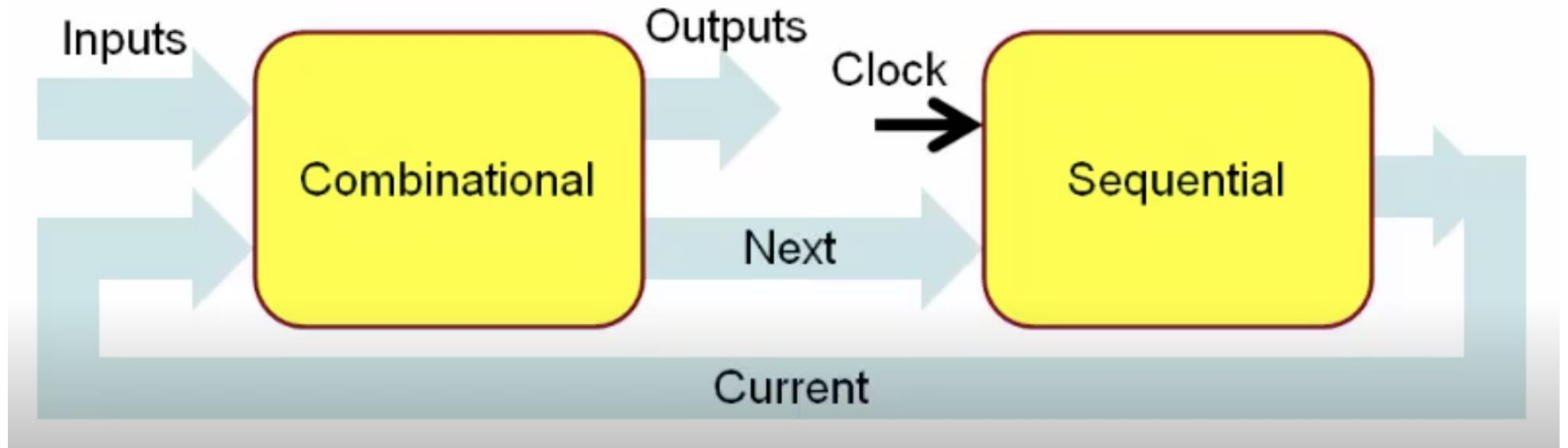


Tb_counter_divider

 



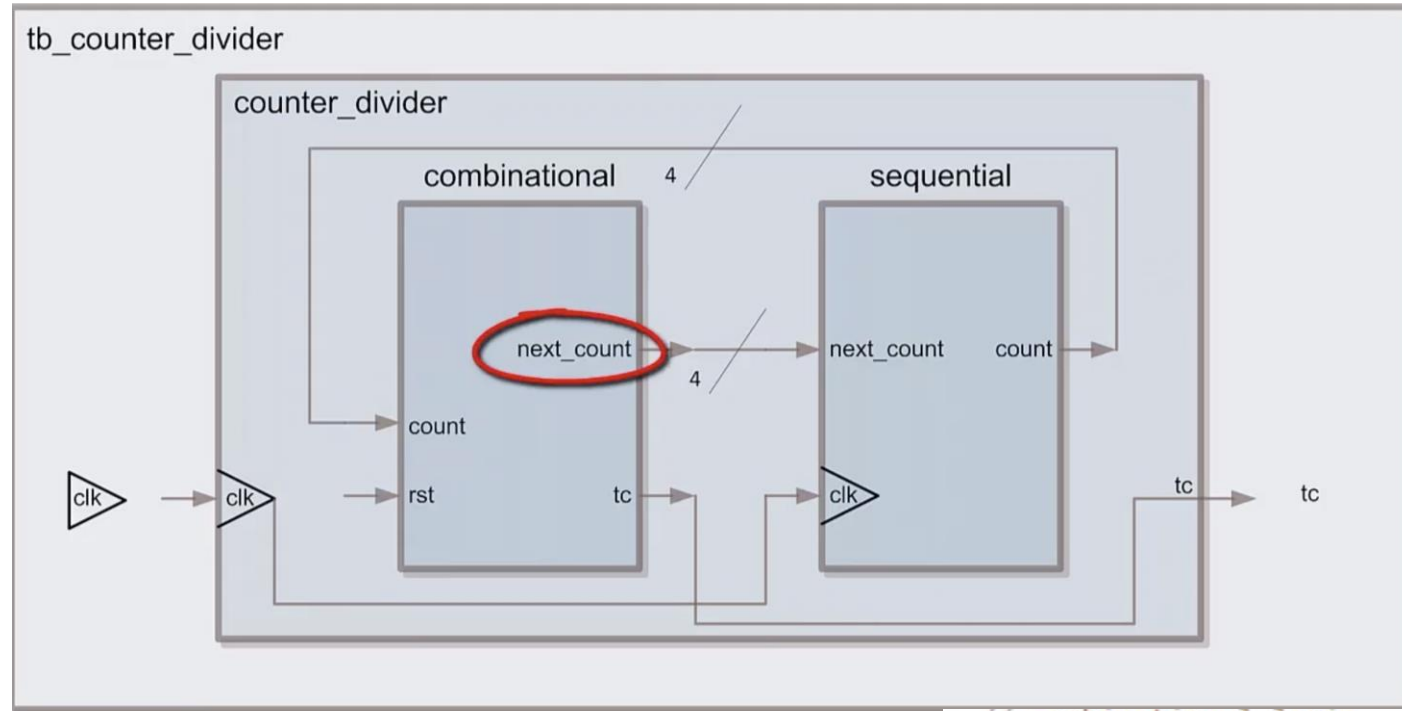
Counter_divider with reset (priority logic)



```
// combinational logic
always @* begin
    if (rst == 1) next_count = 0;
    // defaults
    tc = 0;
    // count down
    next_count = count - 1;
    if (count == 0) tc = 1; // set tc to 1 if count = 0
end
```

```
// combinational logic
always @* begin
    // defaults
    tc = 0;
    // count down
    next_count = count - 1;
    if (count == 0) tc = 1; // set tc to 1 if count = 0
    // priority logic
    if (rst == 1) next_count = 0;
end
```



Add input_counter to comb logic

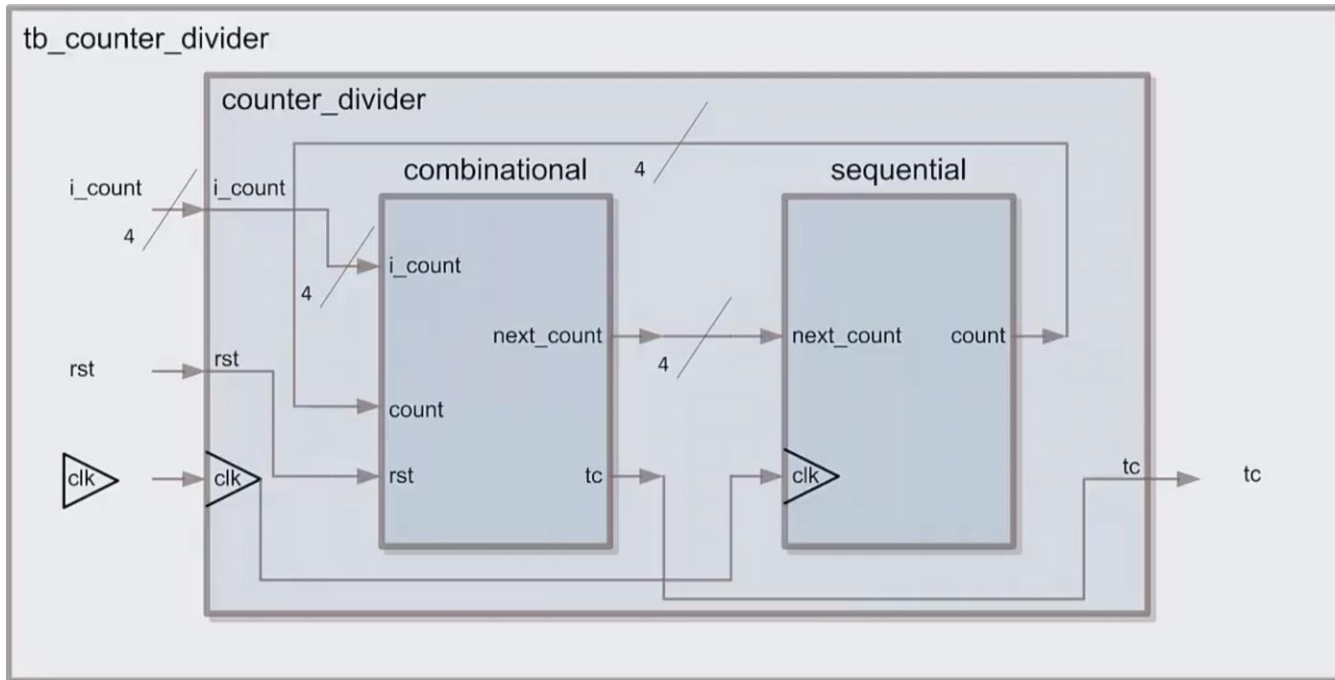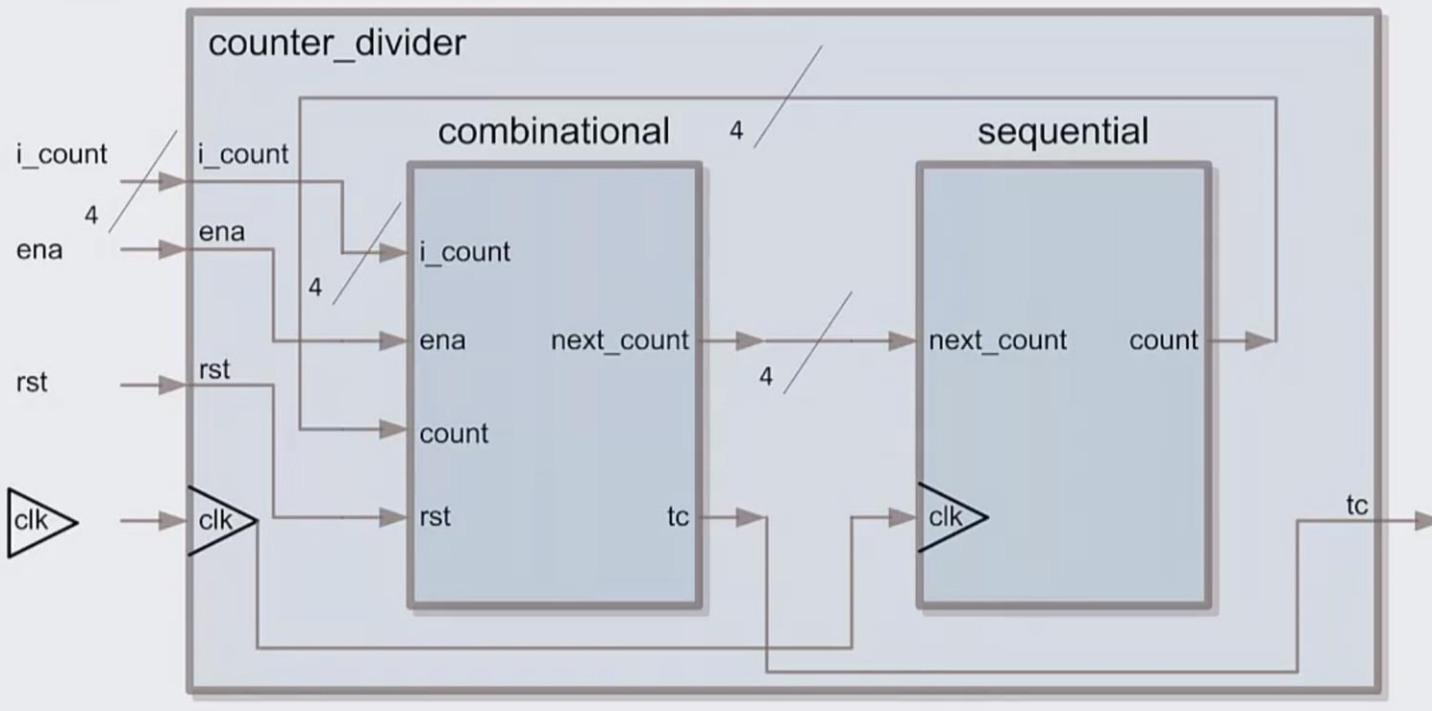

```
always @* begin
    // defaults
    tc = 0;
    // count down
    next_count = count - 1;
    if (count == 0) begin
        tc = 1; // set tc to 1 if count = 0
        next_count = i_count; // and initialize to i_count
    end
    // priority logic
    if (rst == 1) begin
        next_count = 0;
        next_count = i_count; // and initialize to i_count
    end
end
```

Counter_divider with ena

tb_counter_divider



```
// combinational logic
always @* begin
    // defaults
    tc = 0;
    next_count = count; // hold the count
    if (ena == 1) begin
        // count down
        next_count = count - 1;
        if (count == 0) begin
            tc = 1; // set tc to 1 if count = 0
            next_count = i_count; // and initialize to i_count
        end // end of count = 0 if
    end // end of enable if
    // priority logic
    if (rst == 1) begin
        next_count = 0;
        next_count = i_count; // and initialize to i_count
    end
end
end
```

Parameter - BITSIZE


```
module counter_divider #(parameter BIT_SIZE=4)
    (output reg tc, input wire clk, input wire rst,
     input wire [BIT_SIZE-1:0] i_count, input wire ena);

    reg [BIT_SIZE-1:0] count, next_count;


    // synchronous logic
    always @(posedge clk) begin
        count <= next_count;
    end

    // instantiate the uut
    counter_divider #(.BIT_SIZE(3)) uut
        (.tc(), .clk(clk), .rst(rst), .i_count(3'd4), .ena(ena));
endmodule
```

A complete counter_divider

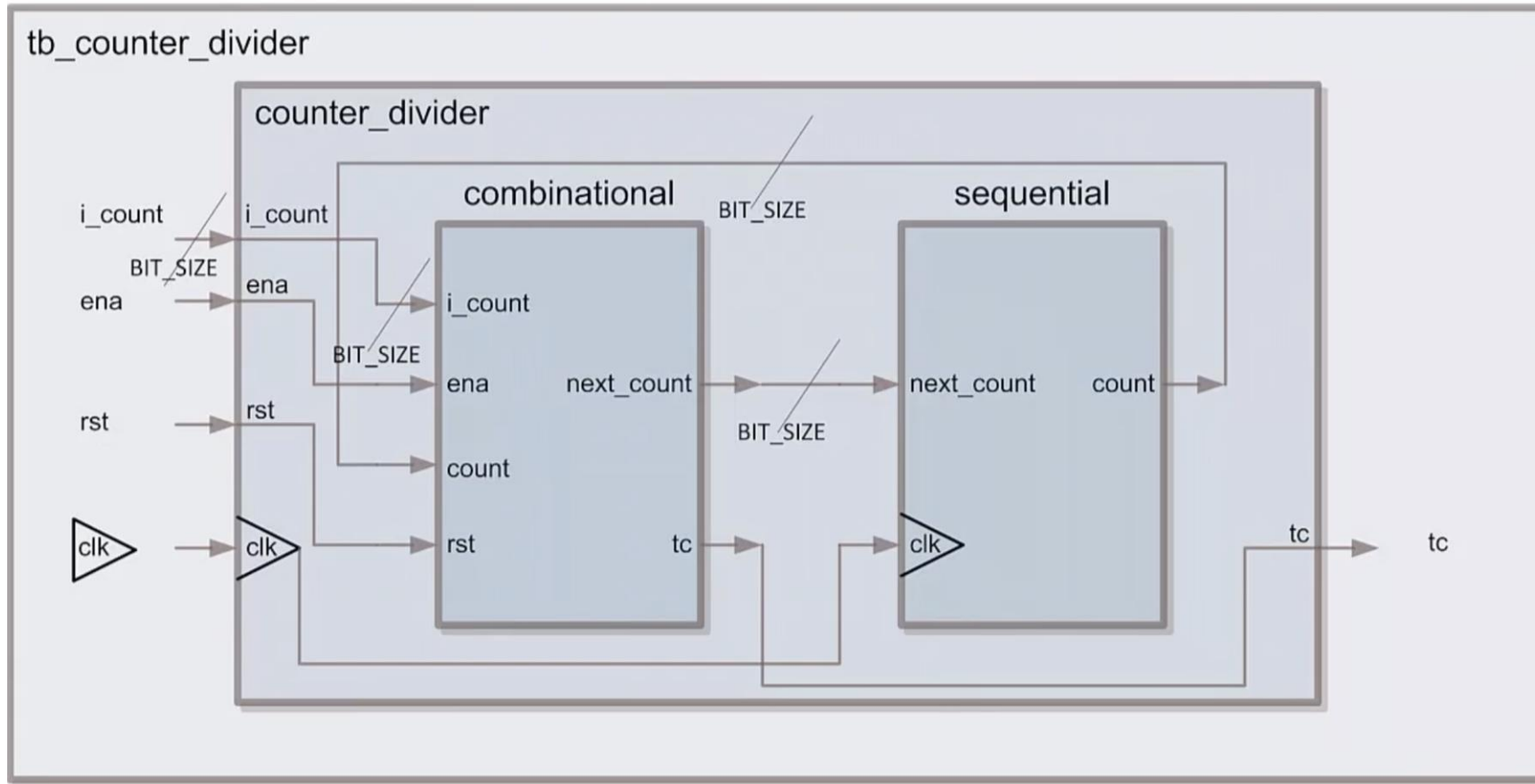

Counter Block Diagram

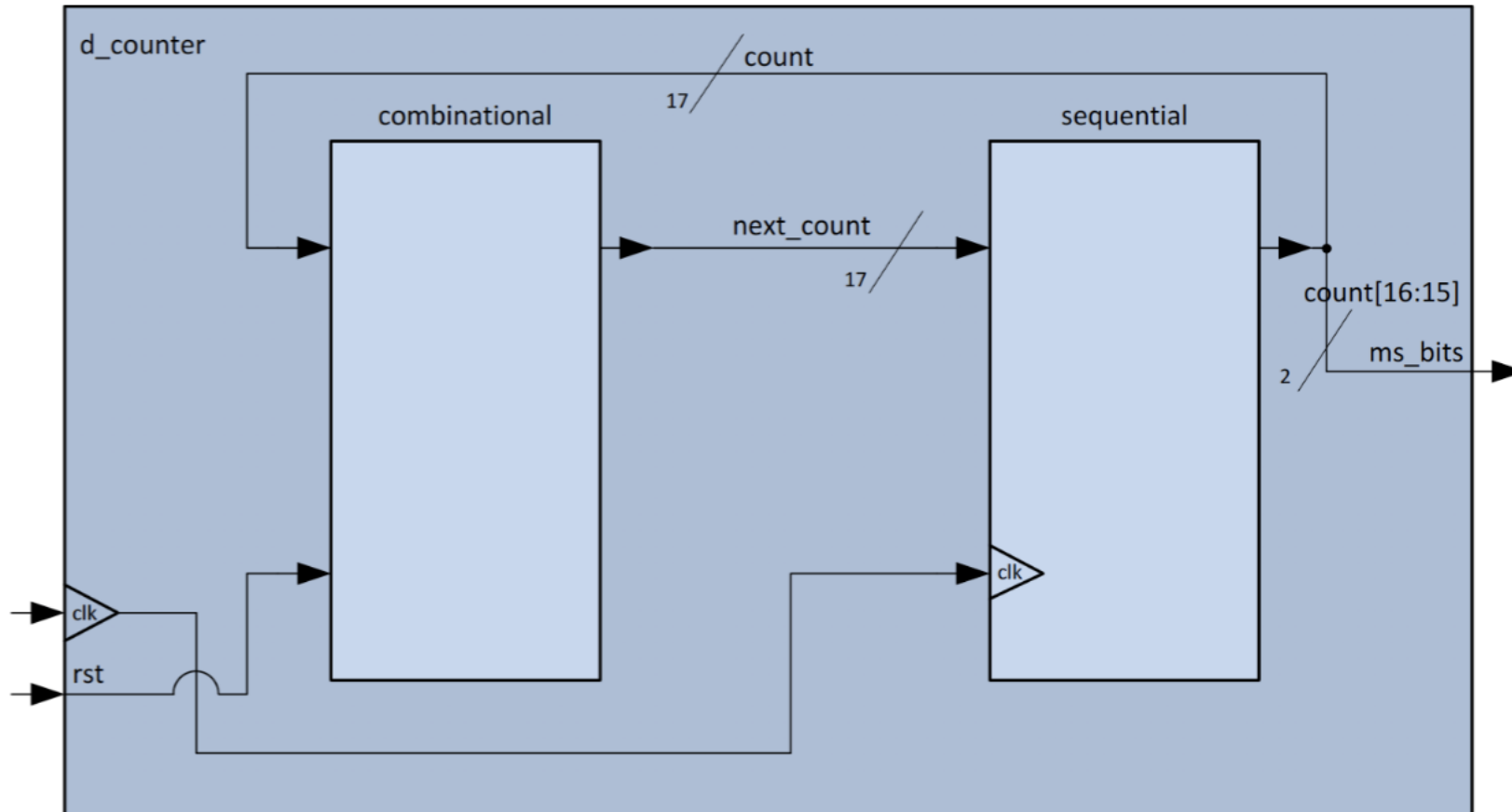

```
// Code your design here
`timescale 1ns/1ns
module cd_counter(output reg ms_bits, input wire clk, input wire rst);


    reg [16:0] count, next_count;

    // synchronous logic
    always @(posedge clk) begin
        count <= next_count;
    end


    // combinational logic
    always @* begin
        // defaults
        // count down
        next_count = count - 1;
        // priority logic
        if (rst == 1) next_count = 0;
    end

    assign ms_bits=count[16:15];
endmodule
```


Ripper counter

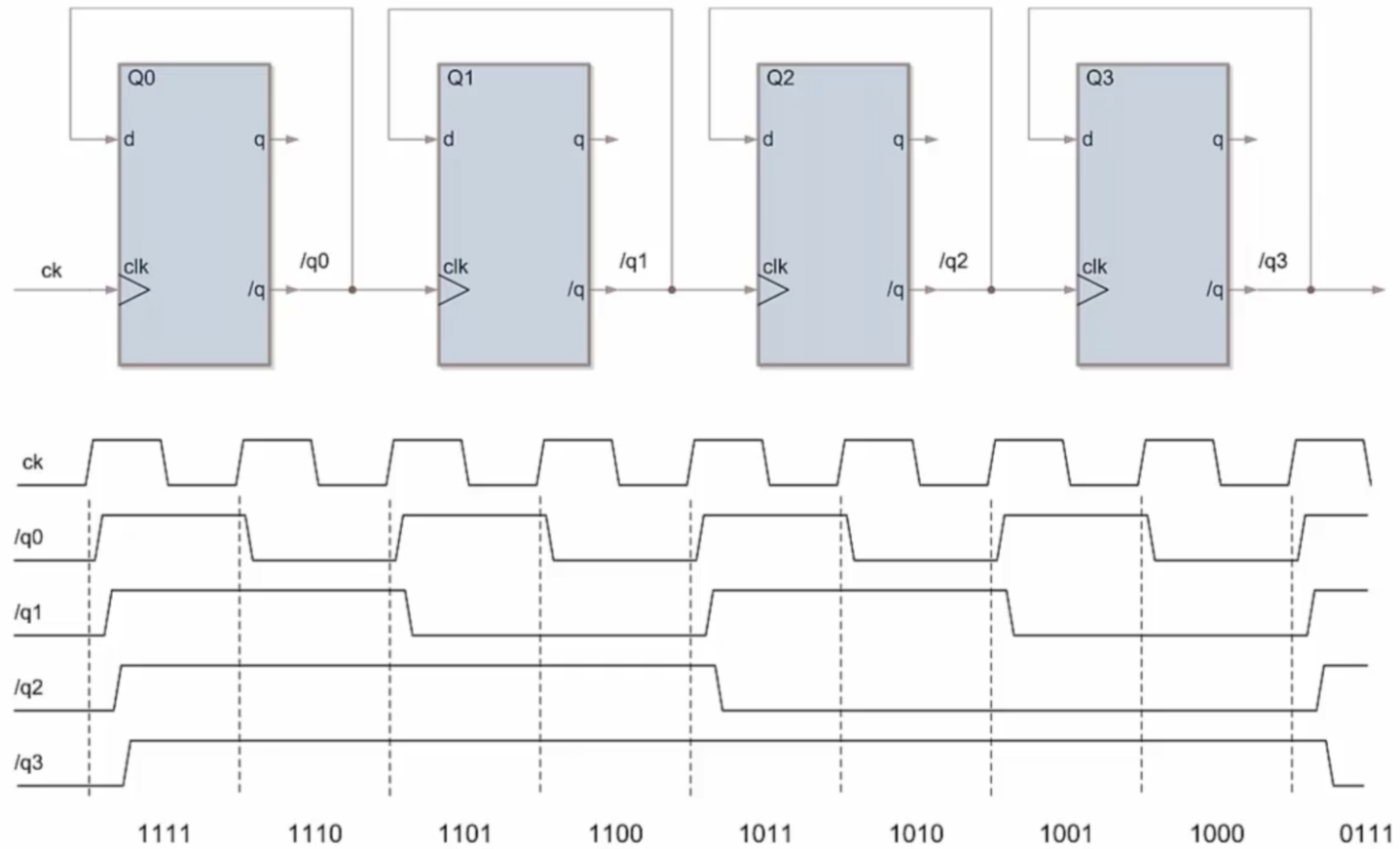

Shift register

 

Circular shift using multiplexer

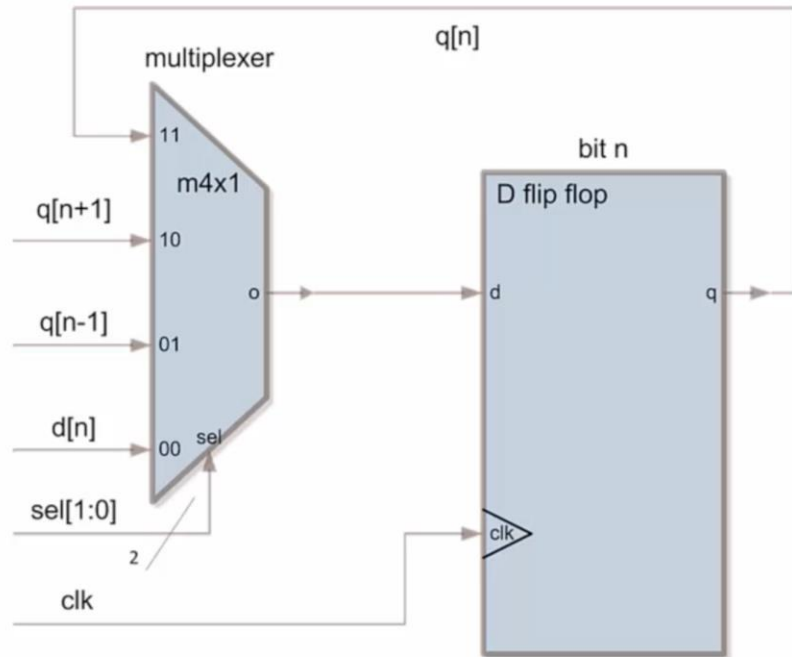

```

1 00_1000_1000 // load
2 01_0000_0100 // rotate down
3 01_0000_0010 // rotate down
4 01_0000_0001 // rotate down
5 01_0000_1000 // rotate down

// combinational logic
always @* begin
    // just a simple mux, since the select is fully deco
    case (sel)
        2'b00: next_q = d; // load from the d port
        2'b01: next_q = {q[0],q[3:1]}; // rotate down
        2'b10: next_q = {q[2:0],q[3]}; // rotate up
        2'b11: next_q = q; // hold
    endcase
end
15 01_0000_0011 // rotate down
16 01_0000_1001 // rotate down

```


Lookup an IC

- <https://www.designfast.com/>
- 4-bit counter

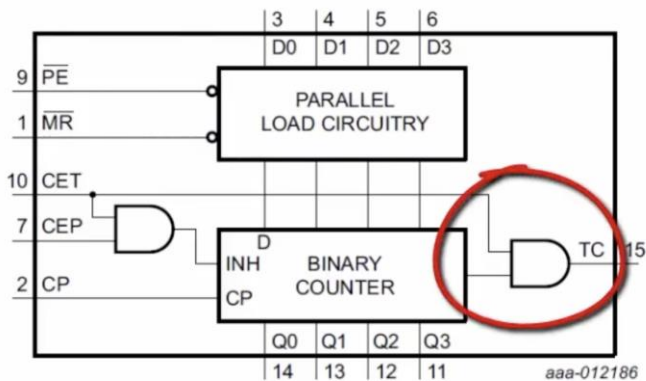


Fig 1. Functional diagram


 


Fig 2. Logic symbol

 

How to use to module counter

 


Fig 15. Modulo-5 counter

 


Fig 16. Modulo-11 counter